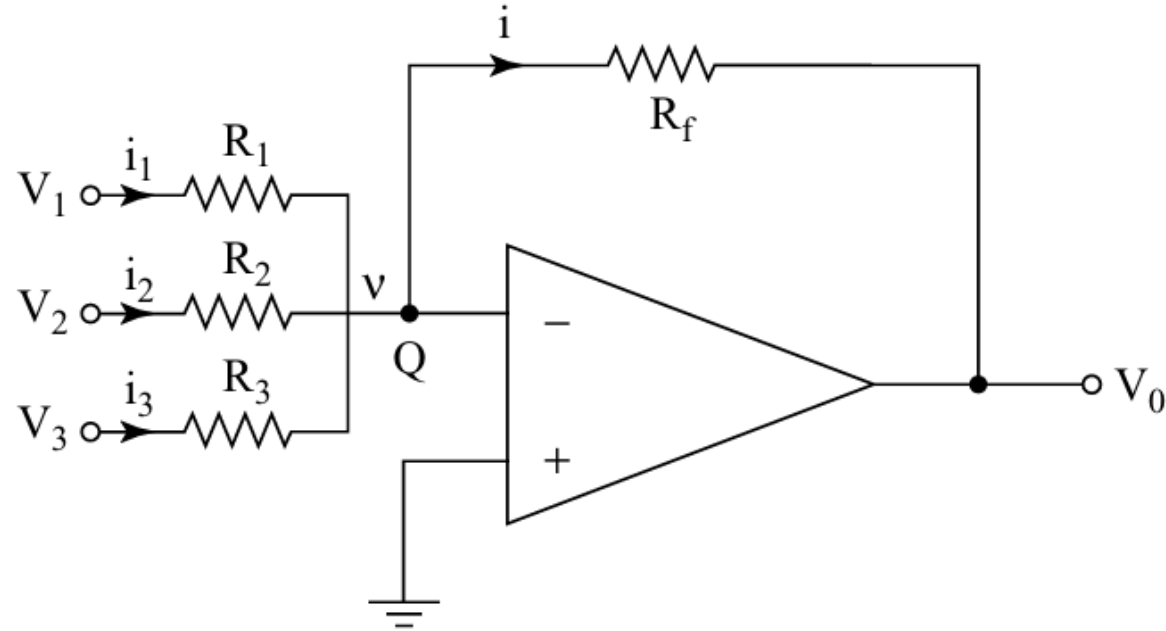


Applications of Operational Amplifiers

By : Dr. Atul R. Phadke

Associate Professor in Electrical Engineering
COEP Technological University Pune (Maharashtra)

OP-AMP AS SUMMING AMPLIFIER:




Assuming point Q at potential v , and assuming no current flowing through the amplifier (infinite input impedance) –

$$i_1 + i_2 + i_3 = i$$
$$\therefore \frac{V_1 - v}{R_1} + \frac{V_2 - v}{R_2} + \frac{V_3 - v}{R_3} = \frac{v - V_o}{R_f}$$

$$V_o = Av \quad \text{or} \quad v = \frac{V_o}{A}$$

OP-AMP AS SUMMING AMPLIFIER:

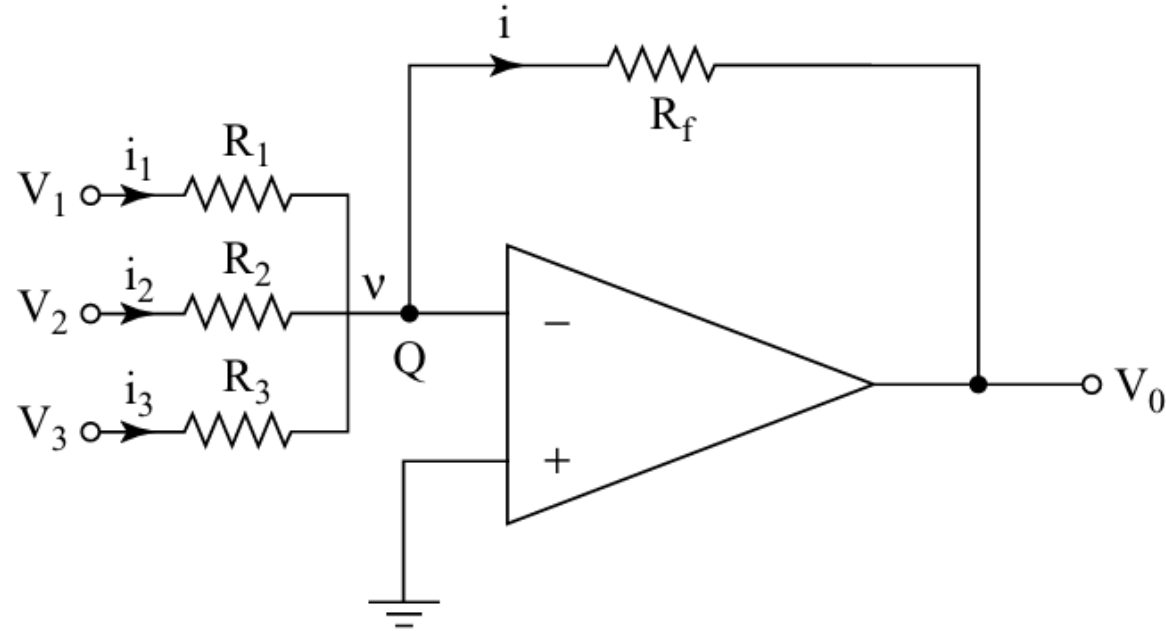


$$\therefore V_o = Av \quad \text{or} \quad v = \frac{V_o}{A}$$

As A tends to ∞ , v tends to zero (virtual ground)

$$\therefore \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = \frac{-V_o}{R_f}$$

$$\therefore V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

OP-AMP AS SUMMING AMPLIFIER:

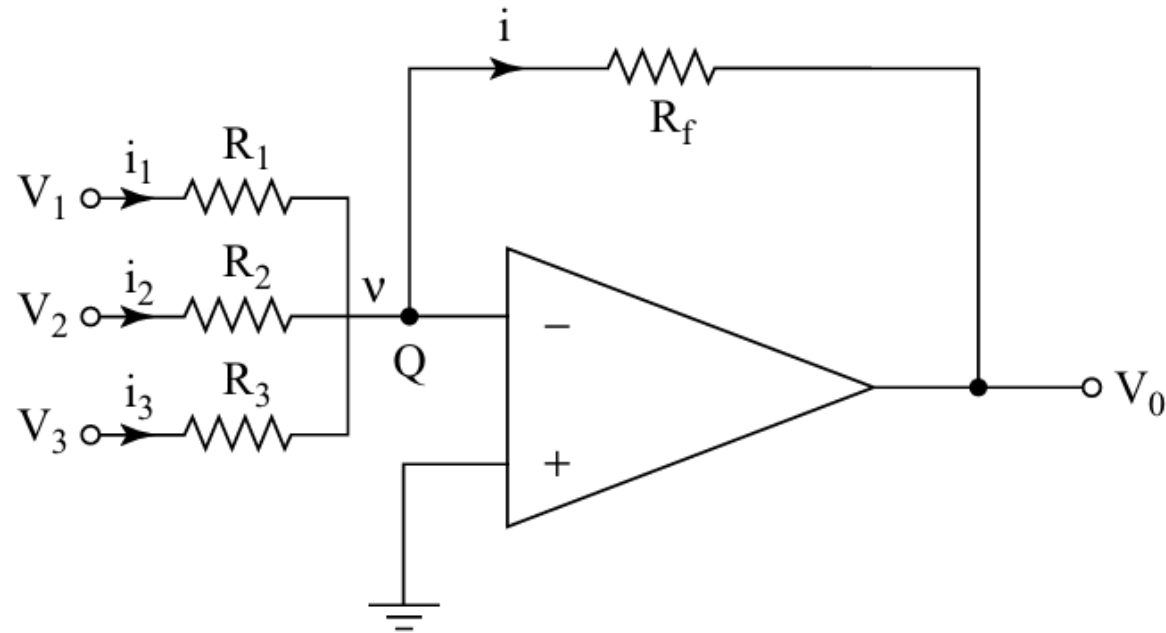

$$\therefore V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

By choosing a suitable ratio of $\frac{R_f}{R}$, the output voltage can be made equal to the sum of the desired ratio of the input voltages.

$$\text{If } R_1 = R_2 = R_3 = R, \quad V_o = -\frac{R_f}{R} [V_1 + V_2 + V_3]$$


$$\text{If } R_f = R, \quad V_o = -[V_1 + V_2 + V_3]$$

EXAMPLE:

Determine the output voltage V_o for the configuration shown in figure,

If $R_1 = R_2 = R_3 = R_f = 1\text{ k}\Omega$

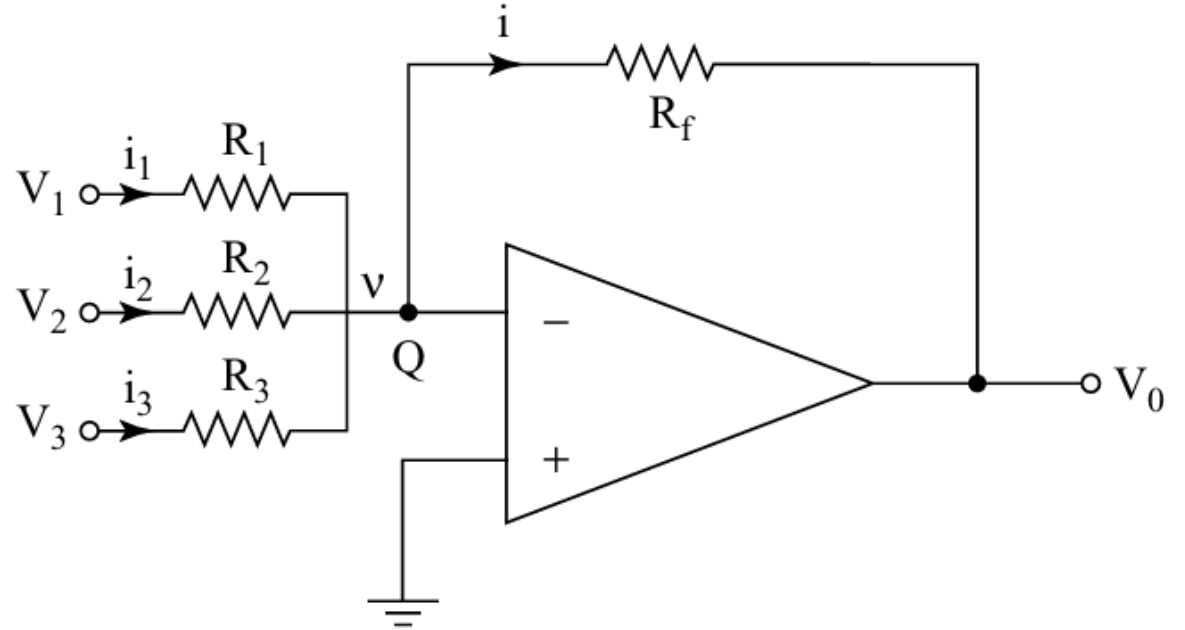$V_1 = +2\text{ V}$, $V_2 = +1\text{ V}$ and $V_3 = +4\text{ V}$



Ans: The circuit is inverting adder (summing) circuit

$$\therefore V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right] = -[V_1 + V_2 + V_3]$$

$$\therefore V_o = -[2 + 1 + 4] = -7\text{ V}$$

OP-AMP AS A SUBTRACTOR:

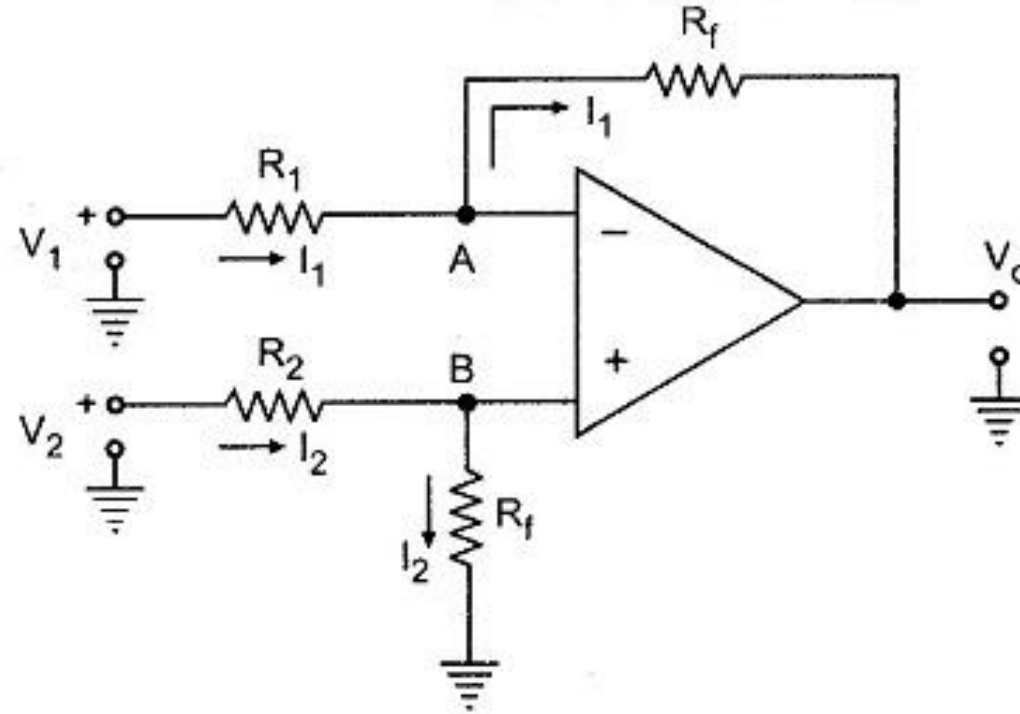




Figure shows a differential amplifier, or a difference amplifier, or simply a subtractor.

Here, the difference between two voltages, i.e., V_2 and V_1 can be amplified using this circuit.

The relation between the inputs and output can be determined using Superposition principle.

Let V_{o1} be the output, with input V_1 acting alone and $V_2 = 0$ to be zero and V_{o2} be the output, with input V_2 acting alone and $V_1 = 0$.

OP-AMP AS A SUBTRACTOR:

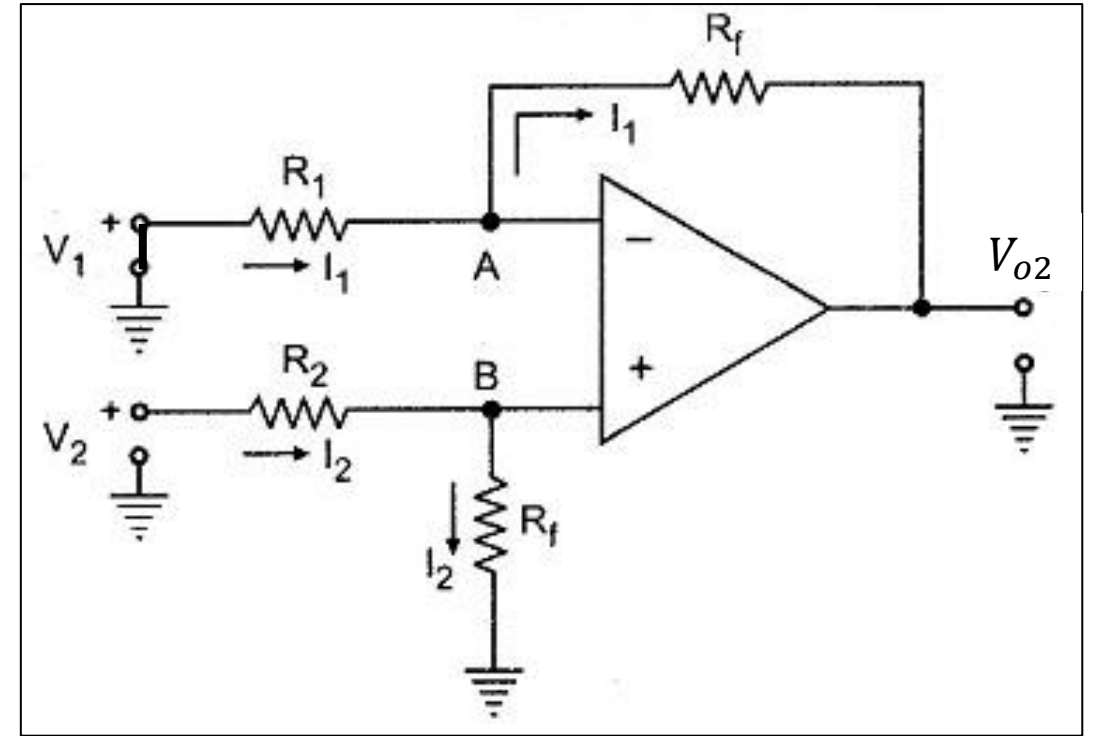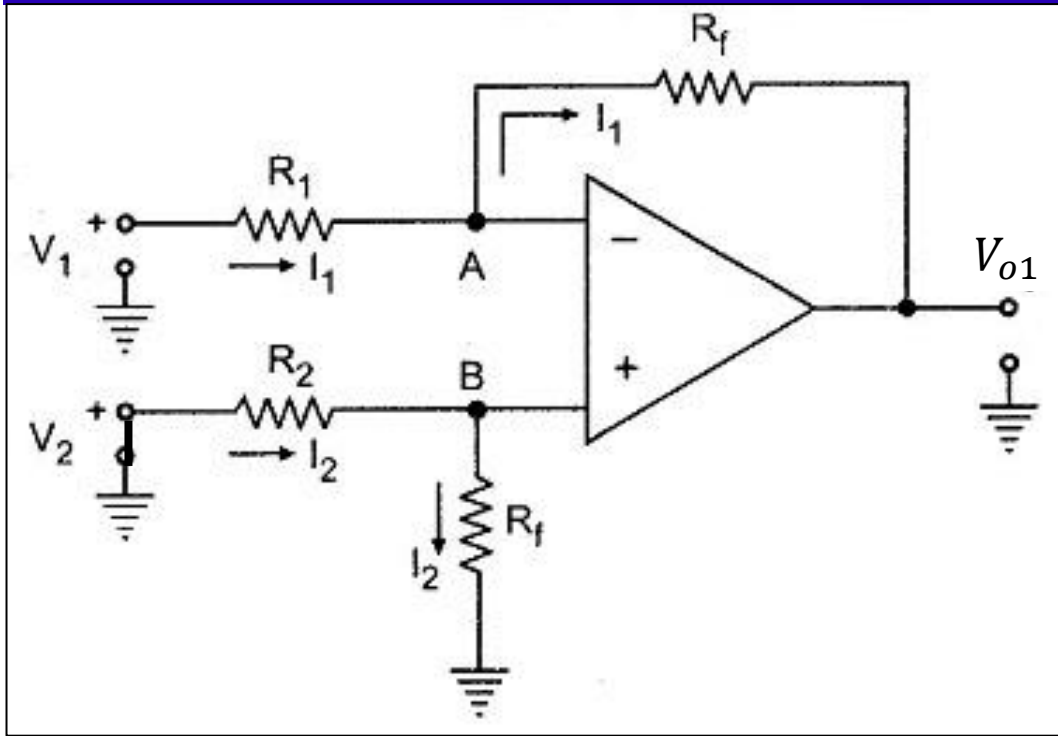



With $V_2 = 0$, the circuit acts as an inverting amplifier. Hence, we can write –

$$V_{o1} = -\frac{R_f}{R_1} V_1 \quad \dots (1)$$

With $V_1 = 0$, the circuit acts as a noninverting amplifier. Hence, we can write –

$$V_{o2} = \left(1 + \frac{R_f}{R_1}\right) V_B \quad \dots (2)$$

OP-AMP AS A SUBTRACTOR:

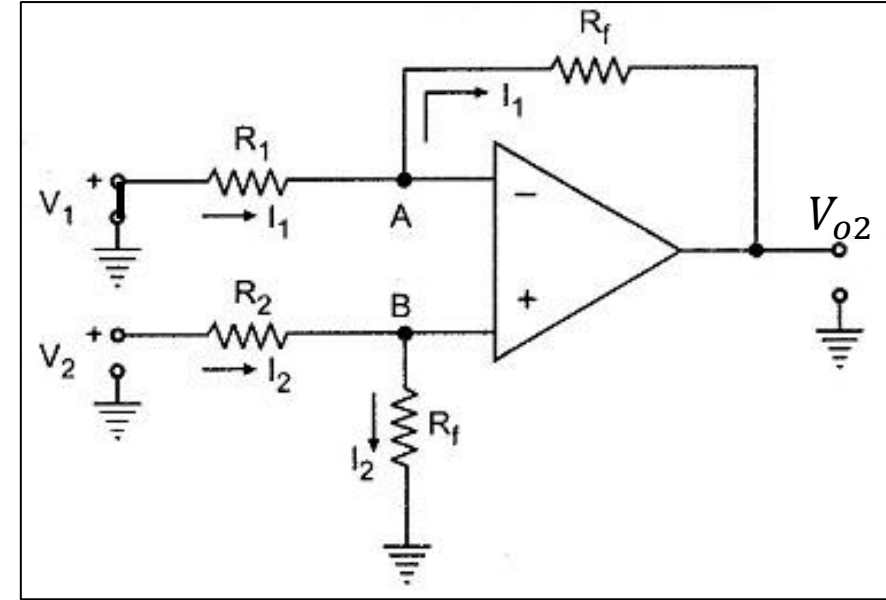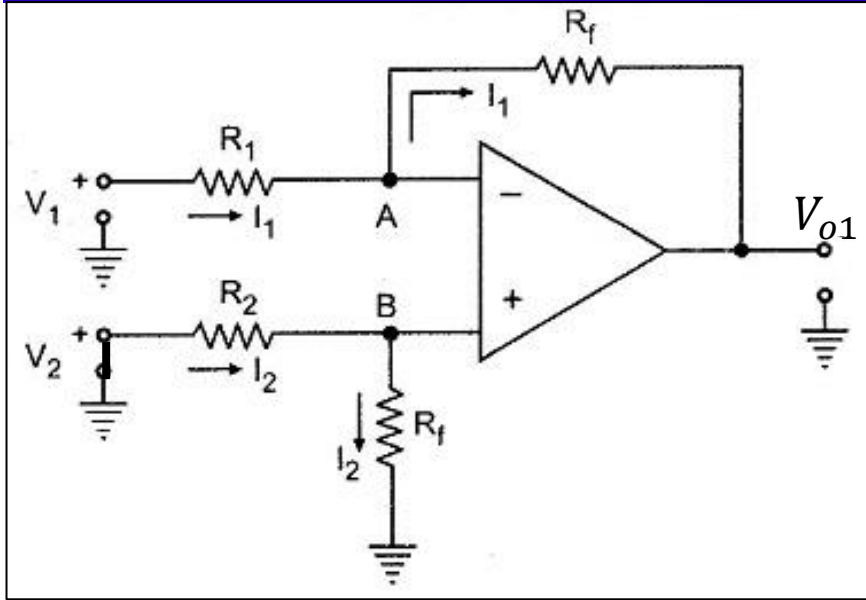



$$I_2 = \frac{V_2}{(R_2 + R_f)} \quad \dots (3)$$

$$\therefore V_B = I_2 \times R_f = \frac{V_2}{(R_2 + R_f)} R_f \quad \dots (4)$$

Substituting V_B in equation (2)

$$V_{O2} = \left[1 + \frac{R_f}{R_1} \right] \left[\frac{R_f}{R_2 + R_f} \right] V_2 \quad \dots (5)$$

OP-AMP AS A SUBTRACTOR:

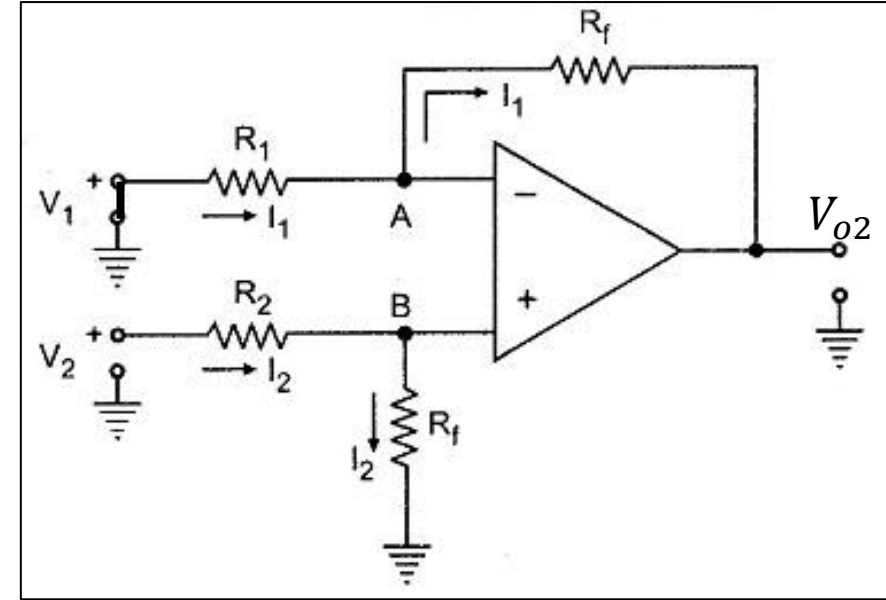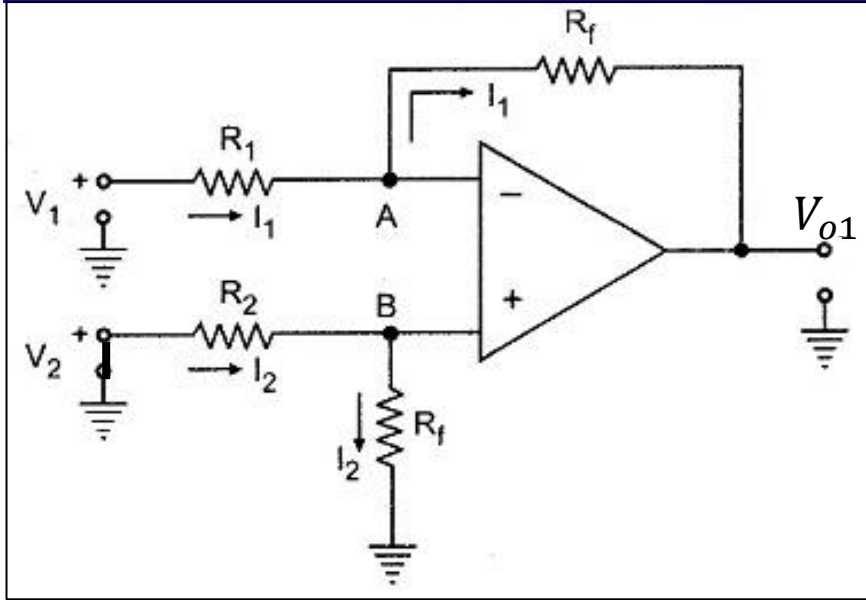

Using superposition principle,



$$V_o = V_{o1} + V_{o2} \quad \dots (6)$$

$$V_o = -\frac{R_f}{R_1} V_1 + \left[1 + \frac{R_f}{R_1} \right] \left[\frac{R_f}{R_2 + R_f} \right] V_2 \quad \dots (7)$$

Now if the resistances are selected as $R_1 = R_2$,

$$V_o = -\frac{R_f}{R_1} V_1 + \left[1 + \frac{R_f}{R_1} \right] \left[\frac{R_f}{R_1 + R_f} \right] V_2 = -\frac{R_f}{R_1} V_1 + \frac{R_f}{R_1} V_2 \quad \dots (8)$$

OP-AMP AS A SUBTRACTOR:

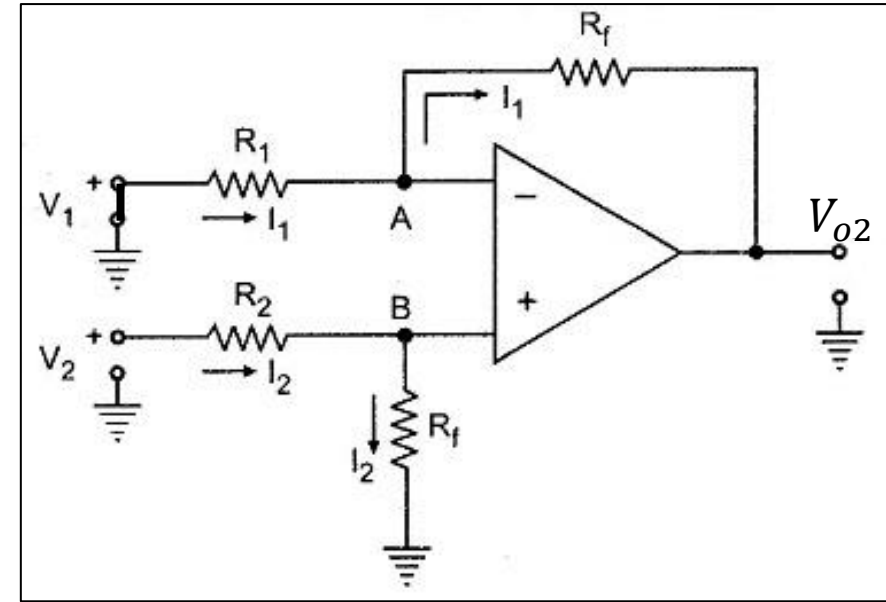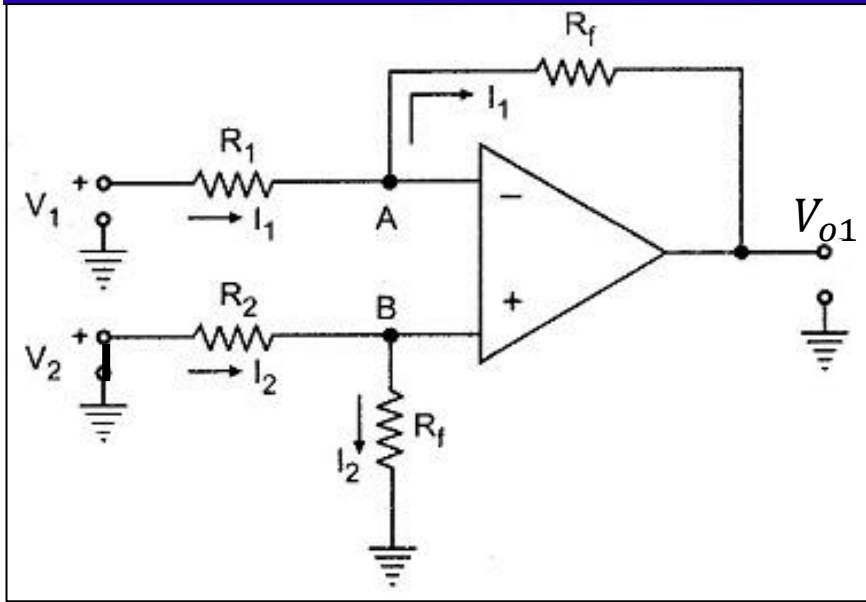



$$V_o = -\frac{R_f}{R_1} V_1 + \left[1 + \frac{R_f}{R_1} \right] \left[\frac{R_f}{R_1 + R_f} \right] V_2 = -\frac{R_f}{R_1} V_1 + \frac{R_f}{R_1} V_2 \quad \dots (8)$$

$$\therefore V_o = +\frac{R_f}{R_1} (V_2 - V_1) \quad \dots (9)$$

Thus, the output voltage is proportional to the difference between the two input voltages.

The circuit acts as a Subtractor using Op-Amp or difference amplifier.

OP-AMP AS A SUBTRACTOR:

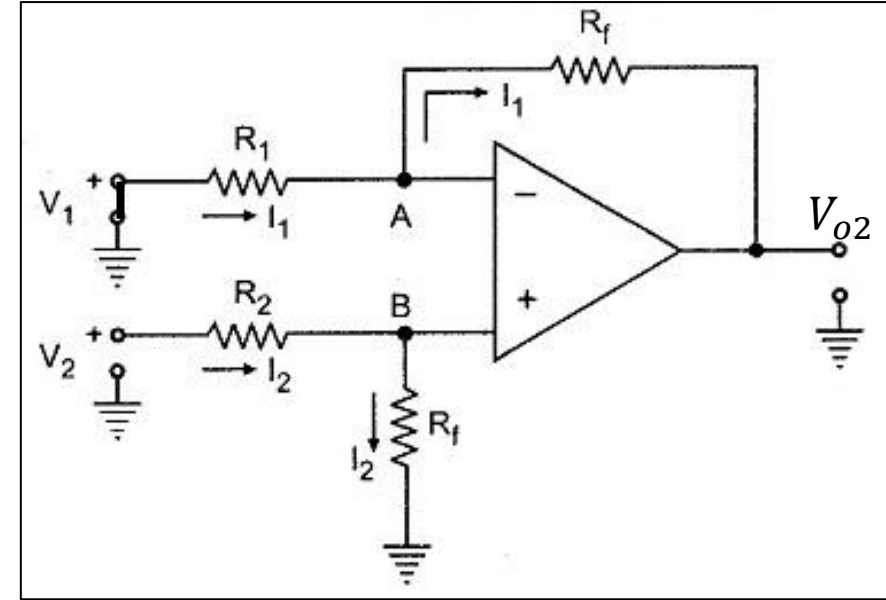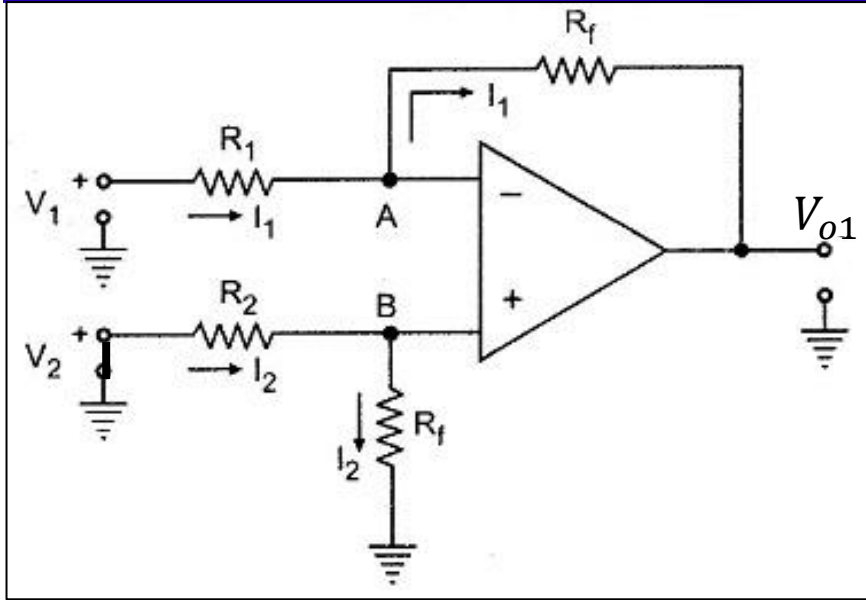

$$\therefore V_o = +\frac{R_f}{R_1} (V_2 - V_1) \quad \dots (9)$$

$$\text{If } R_1 = R_2 = R_f$$

$$V_o = (V_2 - V_1) \quad \dots (10)$$

By selecting proper values of R_1 , R_2 , and R_f , we can obtain the subtraction of two inputs with appropriate strengths like –

$$V_o = aV_2 - bV_1 \quad \dots (11)$$

OTHER APPLICATIONS OF OP-AMP:

There are many applications of op-amps in the field of electronics.

Some of them are mentioned below:

- 1) Current to voltage converter where the output voltage is proportional to the input current.
- 2) Digital to analog converter.
- 3) Analog computer which is constructed by using op-amp integrators and adders to solve differential equations.
- 4) Waveform generators or function generators.
- 5) Oscillators: The oscillators are used to generate repetitive alternating current and voltage waveforms of fixed amplitude and frequency.
- 6) Filters: Filters pass a specified band of frequencies and block signals of frequencies outside this band.

Thank You