



END Semester Examination

Programme: B. Tech

Course Code: ES-04

Branch: Mechanical Group

Duration: 3 Hrs

Student PRN No.

Semester: I

Course Name: BEE

Academic Year: 2023-24

Max Marks: 60

--	--	--	--	--	--	--	--

Instructions:

- Figures to the right indicate the full marks.
- Mobile phones and programmable calculators are strictly prohibited.
- Writing anything on question paper is not allowed.
- Exchange/Sharing of stationery, calculator etc. is not allowed.
- Write your PRN Number on Question Paper.

			Marks	CO	PO
Q1	a)	Use Norton's theorem to calculate the current flowing through the 20 Ω resistor.	6	1, 2	1-4
	b)	Find the value of R_L for which the power transferred to R_L is maximum and find the value of this maximum power.	6	1, 2	1-4
Q2	a)	A 230 V, 50 Hz voltage is applied to a coil $L = 5$ H and $R = 2 \Omega$ is in series with a capacitance C . What value must C have in order that the voltage across the coil be 400 V?	6	1, 2	1-4
	b)	A balanced star connected load has an impedance of $(2 + j3.46) \Omega$ between line and neutral. If the voltage across phase R and neutral be $20\angle-30^\circ$ volts, find current in phases Y and B. What is the voltage from line Y to neutral. Also obtain V_{RB} .	6	1, 2	1-4

$I_{SC1} = 20A \text{ (down)} \text{ --- ①}$
 $I_{SC} = 10A \text{ (down)} \text{ --- ②}$
 $R_N = 10\Omega \text{ --- ①}$
 $I_L = 5.33A \text{ --- ①}$

$R_L = R_i = 6\Omega \text{ --- ②}$
 $I_{L2} = 1.25A \text{ (down)} \text{ --- ③}$
 $P_{max} = 9.375W \text{ --- ①}$

$2) a)$
 $Z_{coil} = 1571\Omega \text{ --- ①}$
 $I = 0.2547A \text{ --- ①}$
 $Z_{eq} = 903\Omega \text{ --- ①}$
 $X_C = 667\Omega \text{ --- ①}$
 $C = 4.7\mu F \text{ --- ②}$

$21 b) Y_{RN} = 20\angle-30^\circ V$
 $Z_{ph} = 2 + j3.46$
 $\cong 4\angle60^\circ$

$I_{RN} = \frac{20\angle-30^\circ}{4\angle60^\circ} = 5\angle-90^\circ A \text{ --- ①}$

$I_{YN} = 5\angle(30-120) = 5\angle-90^\circ A \text{ --- ①}$
 $I_{BN} = 5\angle-210^\circ A \text{ --- ①}$

$V_{YN} = 20\angle-150^\circ V \text{ --- ①}$
 $V_{BN} = 20\angle-270^\circ V \text{ --- ②}$

$V_{RB} = \sqrt{3} V_{ph} = 34.64\angle0^\circ \text{ --- ①}$

Q3	a)	Three impedances $(4 - j6) \Omega$, $(6 + j8) \Omega$ and $(5 - j3) \Omega$ are connected in parallel. Calculate the current in each branch when the total supply current is 20 A.	6	1, 2	1-4
	b)	An iron ring of circular cross-section of $5 \times 10^{-4} \text{ m}^2$ has a mean circumference of 2 m. It has a saw-cut of $2 \times 10^{-3} \text{ m}$ length and is wound with 800 turns of wire. Determine the exciting current when the flux in the air gap is $0.5 \times 10^{-3} \text{ Wb}$. μ_r of iron = 600 and assume areas of air gap and iron are same.	6	2	1-4
Q4	a)	A 1 kVA, single-phase transformer has an iron loss of 20 W and a full load copper loss of 40 W. Calculate its efficiency at (i) full load with p.f. of 0.8 lagging, (ii) half load unity power factor.	6	3	1-4
	b)	Draw schematic diagrams of DC shunt, DC series and DC compound motors and mention their applications.	6	4	1-4
Q5	a)	What is the function of switch fuse unit? State any two advantages and disadvantages of fuses.	4	5	1-4
	b)	Explain the use of MCB and ELCB in electrical wiring installations. Also give their typical specifications.	4	5	1-4
	c)	A residential flat has the following average electrical consumptions per day: 1) 4 tube lights of 20 watts working for 4 hours per day. $\rightarrow 0.32 \text{ kWh}$ 2) 1 water heater rated 1.5 kW working for 1 hour per day. $\rightarrow 1.5 \text{ units}$ 3) 1 water pump of 0.5 kW rating working for 2 hours per day. $\rightarrow 1 \text{ unit}$ 4) 2 fans of 60 W rating working for 8 hours per day. $\rightarrow 0.96 \text{ unit}$ Calculate the cost of energy per month (30 days) if 1 kWh of energy (i.e., 1 unit of energy) costs Rs. 6.	4	1, 5	1-4

3>a) $Y = Y_1 + Y_2 + Y_3 = 0.284 + j0.123 \text{ — ②}$
 $= 0.31 \angle 23.4^\circ$
 $V = 64.5 \angle -23.4^\circ \text{ — ①}$
 $I_1 = V Y_1 = 8.9 \angle 32.79^\circ \text{ A — ①}$
 $I_2 = V Y_2 = 6.45 \angle 76.5^\circ \text{ A — ①}$
 $I_3 = V Y_3 = 11.03 \angle 7.5^\circ \text{ A — ①}$
 $Z_1 = 0.077 + j0.115 \Omega$, $Z_2 = 0.06 - j0.08 \Omega$
 $Z_3 = 0.147 + j0.088 \Omega$

4) a) $\eta_{F.L.} = 93.02\% \text{ — ③}$
 $\eta_{H.L.} = 94.34\% \text{ — ③}$
 b) Schematic diagram $\rightarrow 1 \text{ mark each}$
 Application $\rightarrow 1 \text{ mark each}$


5>a) function \rightarrow switch fuse unit $\rightarrow ②$
 Advantage & disadvantages $\rightarrow 1 \text{ mark each}$
 b) MCB use $\rightarrow ①$, ELCB $\rightarrow ①$
 Specification $\rightarrow ②$

3>b) $S_1 = 5.29 \times 10^6 \text{ AT/Wb — ①}$
 $S_2 = 3.18 \times 10^6 \text{ AT/Wb — ①}$
 $S = S_1 + S_2$
 $S = 8.48 \times 10^6 \text{ AT/Wb — ②}$
 $I = 5.3 \text{ A — ②}$

$S = \frac{NI}{\delta}$ $\therefore I = \frac{S\delta}{N}$


5>c) $= 30 \left[(4 \times \frac{20}{1000} \times 4) + (1 \times 1.5 \times 1) + (1 \times 0.5 \times 2) + (2 \times \frac{60}{1000} \times 8) \right] \times 6$
 $= \text{Rs. } 580.4 \text{ marks } 2/2$
Rs. 680.4 — 4 marks

Q1 a)

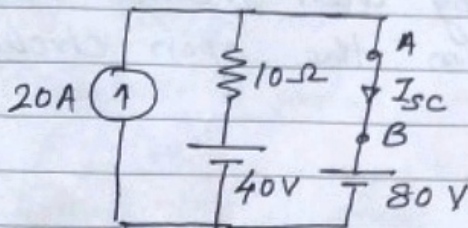

Short circuiting 20Ω res. ... 1 mark

Considering 20 A source acting alone

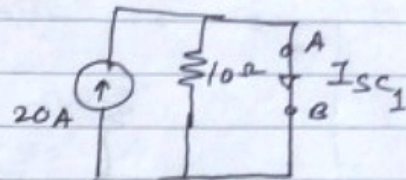


$\therefore I_{sc1} = 20\text{ A}$ from A to B

$I_{sc1} = 20\text{ A}$ (✓) Considering 40 V source acting alone -


Considering 80 V source acting alone

$I_{sc} = 16\text{ A}$ (✓)

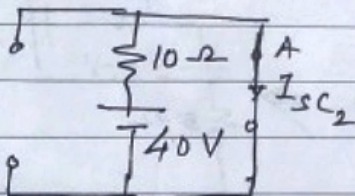

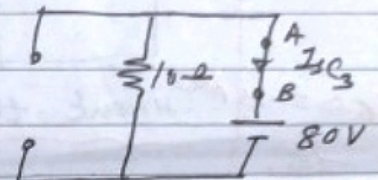(2)

$I_L = 25.83\text{ A}$ (✓) $\therefore I_{sc2} = 40/10 = 4\text{ A}$ from A to B




$\therefore I_{sc3} = 80/10 = 8\text{ A}$ from B to A

Applying superposition principle -


$$I_{sc} = I_N = 20 + 4 - 8 = 16\text{ A from A to B} \quad (2\text{ marks})$$

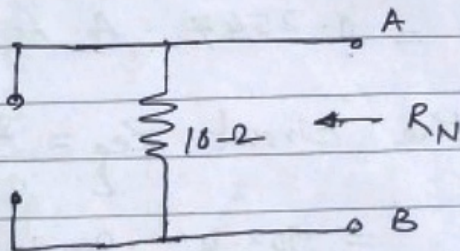Now, removing all sources & replacing by their internal resistances -



$\therefore R_N = 10\Omega$... (1 mark)

\therefore Norton's equivalent circuit -

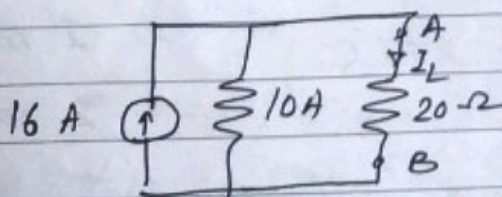


... 1 mark

$$\therefore I_L = 16 \times \frac{10}{10+20}$$

$= 5.33\text{ A from A to B}$

... 1 mark

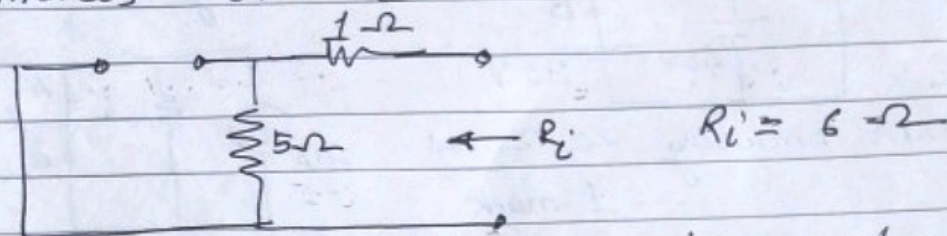Q1 b) Replacing all sources by their internal resistances and looking back from the open circuited terminals of R_L




Power transferred will be maximum when

$$R_L = R_i = 6 \Omega$$

2 marks

$R_L = R_i = 6 \Omega$
②

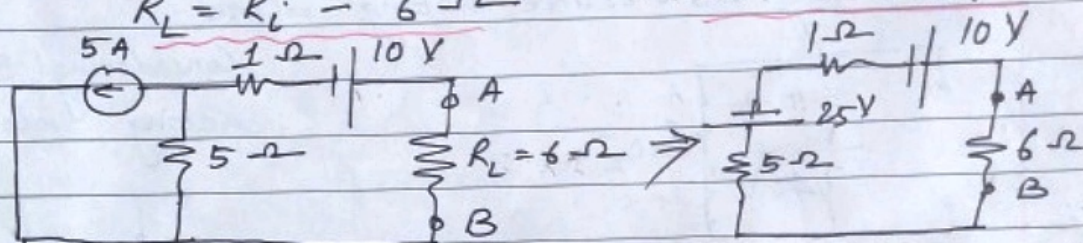

$I_{6\Omega} = 1.25 \text{ A}$
③

Current through 6Ω res. = $\frac{15}{5+6+1} = 1.25 \text{ A}$ from B to A
3 marks

Maximum power = $I^2 R = (1.25)^2 \times 6 = 9.375 \text{ Watt}$... 1 mark
①

Q2 a) Impedance of the coil = $\sqrt{R^2 + X_L^2}$

$$Z_{\text{coil}} = \sqrt{2^2 + (2\pi \times 50 \times 5)^2} = 1570.8 \Omega$$

1 mark

$Z_{\text{coil}} = 1570.8 \Omega$
①

\therefore Current $I = \frac{400}{1570.8} = 0.2547 \text{ A}$... 1 mark

$I = 0.2547 \text{ A}$
①

Total impedance of the circuit $Z_{eq} = \frac{230}{0.2547}$

$$= 903.21 \Omega$$

1 mark

$$Z_{eq} = \sqrt{R^2 + (X_L - X_C)^2} = 903.21 \Omega$$

$$X_C = 667.6 \Omega = \frac{1}{2\pi f C}$$

1 mark

$$\therefore C = 4.77 \mu\text{F}$$

2 marks

b) $V_{RN} = 20 \angle 30^\circ \text{ V}$

$$Z_{ph} = 2 + j3.46 \approx 4 \angle 60^\circ \Omega$$

$$I_{RN} = \frac{20 \angle -30^\circ}{4 \angle 60^\circ} = 5 \angle +30^\circ \text{ A} \quad \dots \text{1 mark}$$

$$\therefore \text{Current in Y phase} = 5 \angle (+30 - 120)^\circ = 5 \angle -90^\circ \text{ A} \quad \dots \text{1 mark}$$

$$\text{Current in B phase} = 5 \angle (-150 - 120)^\circ = 5 \angle -270^\circ \text{ A} \quad \dots \text{1 mark}$$

$$\text{or} = 5 \angle 90^\circ \text{ A}$$

$$20 \angle -150^\circ \quad V_{YN} = 20 \angle (30 - 120)^\circ = 20 \angle -90^\circ \text{ V} \quad \dots \text{1 mark}$$

$$20 \angle -270^\circ \quad V_{BN} = 20 \angle (90 - 120)^\circ = 20 \angle -270^\circ \text{ V} \quad \dots \text{1 mark}$$

$$\text{or} = 20 \angle 150^\circ$$

$$V_{RB} = \sqrt{3} V_{ph} = 34.64 \text{ V}$$

$$V_{RN} + V_{NB} = 34.64 \angle 0^\circ \text{ V} \quad \dots \text{1 mark}$$

Q3a)

$$Z_1 = (4 - j6) \Omega \quad \therefore Y_1 = \frac{1}{(4 - j6)} = 0.077 + j0.115$$

$$Z_2 = (6 + j8) \Omega \quad \therefore Y_2 = \frac{1}{6 + j8} = 0.06 - j0.08$$

$$Z_3 = (5 - j3) \Omega \quad \therefore Y_3 = \frac{1}{5 - j3} = 0.147 + j0.088$$

$$\therefore Y = Y_1 + Y_2 + Y_3 = 0.284 + j0.123 \quad \dots \text{2 marks}$$

$$= 0.31 \angle 23.4^\circ$$

$$\text{Supply voltage } V = \frac{I}{Y} = \frac{20 \angle 0^\circ}{0.31 \angle 23.4^\circ}$$

$$= 64.5 \angle -23.4^\circ \text{ V} \quad \dots \text{1 mark}$$

$$I_1 = V Y_1 = (64.5 \angle -23.4^\circ) (0.077 + j0.115) = (64.5 \angle -23.4^\circ) (0.138 \angle 56.19^\circ) = 8.9 \angle 32.79^\circ \text{ A} \quad \dots \text{1 mark}$$

$$I_2 = V Y_2 = (64.5 \angle -23.4^\circ) (0.06 - j0.08) = (64.5 \angle -23.4^\circ) (0.1 \angle -53.13^\circ) = 6.45 \angle -76.5^\circ \text{ A} \quad \dots \text{1 mark}$$

$$I_3 = V Y_3 = (64.5 \angle -23.4^\circ) (0.147 + j0.088) = (64.5 \angle -23.4^\circ) (0.171 \angle 30.9^\circ) = 11.03 \angle 7.5^\circ \text{ A} \quad \dots \text{1 mark}$$

$$\mu_0 = \frac{B}{H}$$

$$H = \frac{NI}{l}$$

$$NI = Hl \quad \text{from } NI = \frac{\Phi \times l}{\mu_0 \mu_r A}$$

Q3 b) length of iron = $2 - 2 \times 10^{-3}$
 $= 1.998 \text{ m}$

Reluctance of iron path $S_1 = \frac{l_{\text{iron}}}{\mu_0 \mu_r A}$ $l_{\text{iron}} = 2 \text{ m}$
 $l_{\text{gap}} = 2 \times 10^{-3} \text{ m}$

$$S_1 = 5299859.6 \text{ AT/Wb} \text{ --- (1)} \quad = \frac{1.998}{4\pi \times 10^{-7} \times 600 \times 5 \times 10^{-4}}$$

$$S_2 = 3183098.9 \text{ AT/Wb} \text{ --- (1)} \quad = \frac{l_{\text{gap}}}{4\pi \times 10^{-7} \times 1 \times 5 \times 10^{-4}} \quad \text{1 mark}$$

$$S = S_1 + S_2 = \frac{2 \times 10^{-3}}{4\pi \times 10^{-7} \times 1 \times 5 \times 10^{-4}} = 3183098.9 \text{ AT/Wb} \dots 1 \text{ mark}$$

Total reluctance, $S = S_1 + S_2$
 $I = 5.3 \text{ A} \text{ --- (2)} \quad = 8482958.5 \text{ AT/Wb} \dots 2 \text{ marks}$

$$S = \frac{NI}{\Phi} \quad \therefore I = \frac{S \times \Phi}{N}$$

$$I = 5.3 \text{ A} \dots 2 \text{ marks}$$

Q4 a) (i) $\eta_{FL} = \frac{1 \times 1000 \times 1 \times 0.8}{1 \times 1 \times 0.8 + 0.02 + (1)^2 \times 0.04} \times 100$

$$\eta_{FL} = 93.02 \% \dots 3 \text{ marks}$$

$$\eta_{HL} = \frac{0.5 \times 1 \times 1}{0.5 \times 1 \times 1 + 0.02 + (0.5)^2 \times 0.04} \times 100$$

$$\eta_{HL} = 94.34 \% \dots 3 \text{ marks}$$

- b) Schematic diagrams - 1 mark each ✓
 Applications - 1 mark each ✓

- Q5 a) Function of switch-fuse unit - 2 marks
 Advantages and disadvantages - 1 mark each

- b) Use of MCB - 1 mark ✓, ELCB - 1 mark ✓
 Specifications - 2 marks ✓

c) Electricity bill = Units in kWh \times Rate/unit
 $= 30 \left[\left(4 \times \frac{20}{1000} \times 4 \right) + (1 \times 1.5 \times 1) + (1 \times 0.5 \times 2) \right. \\ \left. + \left(2 \times \frac{60}{1000} \times 8 \right) \right] \times 6 = \text{Rs. } 685.4/- \dots 4 \text{ marks}$

$$\text{Rs. } = 545.4$$

(4)