



COEP TECHNOLOGICAL UNIVERSITY, PUNE

Wellesly Road, Shivajinagar, Pune - 411005

Assignment : 04

(Q.1)

Intrinsic semiconductor

- 1) Semiconductor in the pure form is known as intrinsic semiconductor.

Extrinsic semiconductor

The semiconductor, resulting from mixing of impurity in it is known as extrinsic semiconductor.

- 2) Their conductivity is low

Their conductivity is high.

- 3) Electrical conductivity is function of temperature alone

Electrical conductivity is function of temperature as well as no. of doped atoms.

Extrinsic semiconductors are of 2 types Namely,

- (i) P type (ii) N type.

(i) P Type materials are the semiconductor materials doped with a tetravalent impurity.

→ Majority charge carriers are holes.

(ii) N type materials are the semiconductor materials doped with a pentavalent impurity.

→ Majority charge carriers are electrons.



COEP TECHNOLOGICAL UNIVERSITY, PU

Wellesley Road, Shivajinagar, Pune - 411005


g-2

- ⇒ (i) Acceptor type impurities:-
- ⇒ (I) Acceptor impurities increase the hole concentration of semiconductor material.
- (II) they are trivalent impurities and are deficient of electrons.
- ⇒ carriers contributed by them are holes.

(ii) Donor type impurities:-

- (I) Donor impurities increase the electron concentration in the semiconductor material.
- (II) they are tetravalent impurities and are rich of electrons.
- ⇒ carriers contributed by them are electrons.

g-3

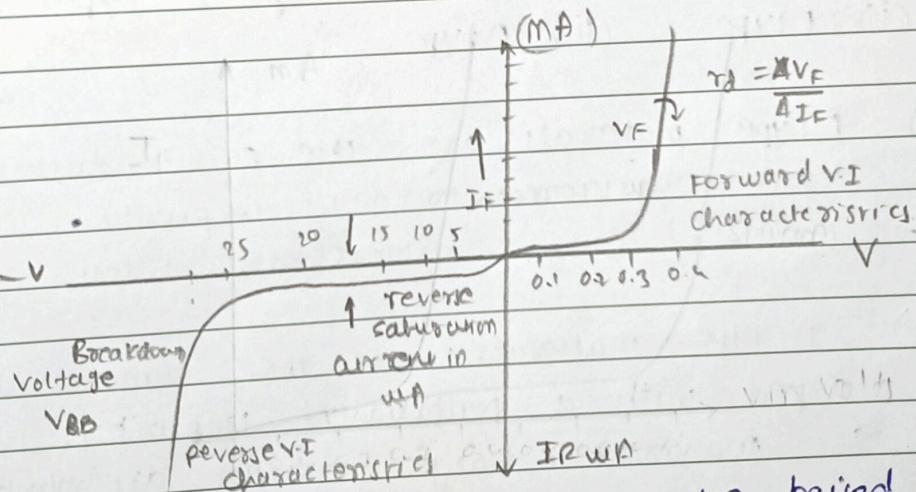

- (i) A junction diode has to be biased in either forward or reverse manner.

- (ii) when a P-N Junction diode is forward biased +ve terminal of the battery will repel



COEP TECHNOLOGICAL UNIVERSITY, PUNE

Wellesly Road, Shivajinagar, Pune - 411005

The holes on the P side and the electrons on the N side will be repelled by the negative terminal of the battery.

(ii) As a result the depletion layer which is created at junction decreases and potential barrier will be reduced.

(iii) Above the barrier potential when the voltage is increased, large amount of current (I_F) flows through the P-N junction.

(iv) This current is known as forward current (I_F)

⇒ An ideal diode is a diode which acts as a perfect conductor in forward bias and a perfect insulator in reverse biased condition.

Q.4 (i) Peak inverse voltage is the highest voltage a semiconductor diode can withstand in reverse bias before it breaks down. It is also known as breakdown voltage.

(ii) Forward biasing :- When negative terminal of battery is connected to 'N' side of semiconductor.

⇒ The current flows in large quantity due to majority charge carriers (electrons).

Reverse biasing :- When negative terminal of battery is connected to 'P' side of semiconductor



COEP TECHNOLOGICAL UNIVERSITY, PUNE

Wellesley Road, Shivajinagar, Pune - 411005

the width of depletion layer and barrier potential increases. due to with semiconductor diode acts as an insulator.

(iii) potential barrier:- when PN junction is formed there is an initial diffusion of electrons and holes.

→ when electrons and holes occupy 2 different sides in a semiconductor a depletion region is generated which creates a potential difference.

(iv) depletion layer:- The layer formed due to diffusion of electrons and holes on the opposite sides.

(v) Reverse saturation current:- The small amount of current which flows through the diode in microamperes . in reverse bias . I_s \propto

Q5) ~~what is~~ zener diode :-

→ zener diode is a heavily doped P-N Junction diode.

→ This diode is specially designed for voltage regulation

→ Forward bias characteristics of a zener diode are same as ordinary diode.




COEP TECHNOLOGICAL UNIVERSITY, PUNE

Wellesly Road, Shivajinagar, Pune - 411005

⇒ But it acts differently under reverse bias conditions.

But it has a very sharp breakdown voltage that the voltage across the zener diode remains almost constant although the current varies by large amounts.

I-V characteristics of zener diode

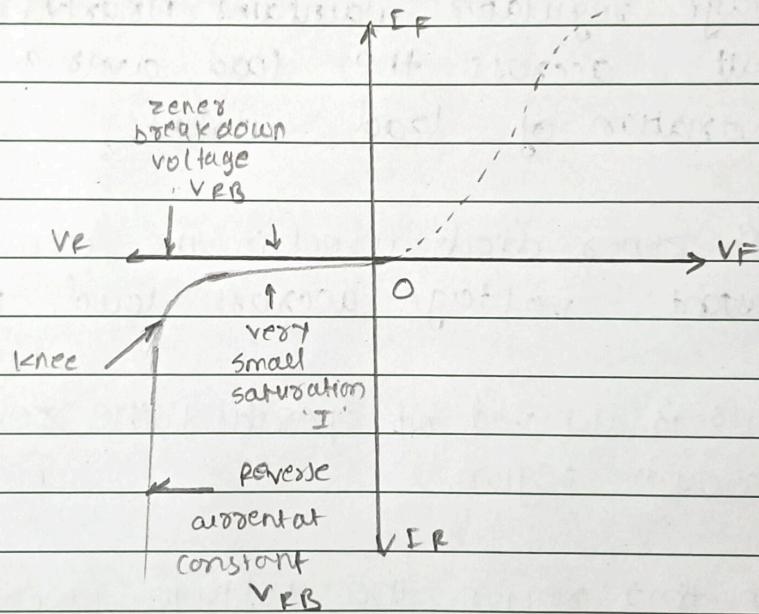

⇒ since it is heavily doped breakdown occurs at very low voltage than ordinary diodes.




COEP TECHNOLOGICAL UNIVERSITY, PUNE

Wellesly Road, Shivajinagar, Pune - 411005

Q.6

Zener diode as a voltage regulator.

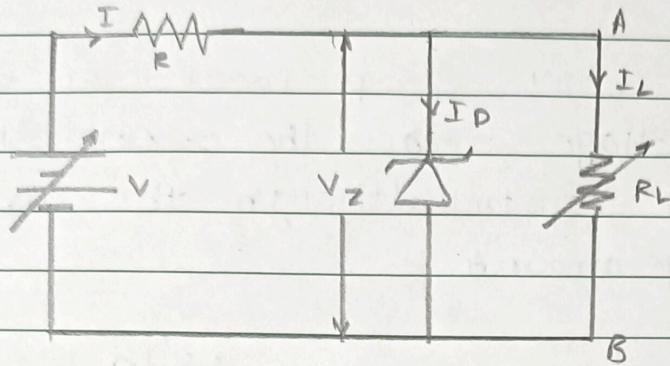


- (i) Voltage regulator maintains nearly constant voltage output across the load over a wide range of variation of load current
- (ii) The zener diode used in the circuit maintains a constant voltage across load terminals A and B
- (iii) This is achieved by operating the zener diode in Breakdown region.
- (iv) In this region the voltage across diode change very slightly over a large variation of zener current.
- (v) Zener breakdown voltage must be lower than applied voltage.



COEP TECHNOLOGICAL UNIVERSITY, PUNE


Wellesly Road, Shivajinagar, Pune - 411005

Q.7) A BJT (Bipolar junction transistor)

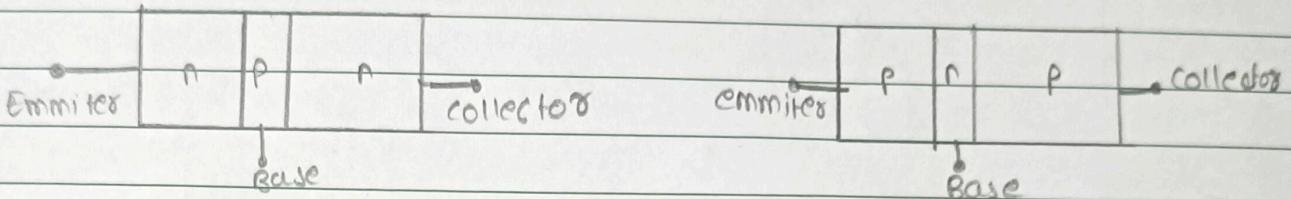

→ Construction:-

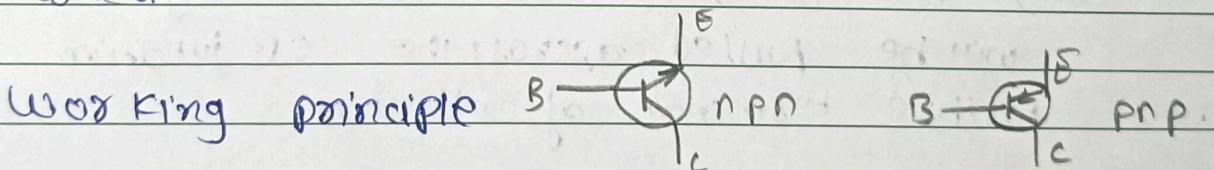- (i) BJT has 3 layers of semiconductor materials.
- (ii) Those layers are arranged either in p-n-p or n-p-n sequence
- (iii) In an n-p-n transistor a p type semiconductor material is sandwiched between 2 n type materials → vice versa for p-n-p.
- (iv) BJT has 2 back to back p-n junctions connected. Back to back means the central layer is called base.
⇒ one of the outer layers which is heavily doped is called emitter and the one lightly doped is called collector.




- (i) In BJT working occurs with the help of active regions.
 - (ii) since there are 2 junctions (i) Emitter - base and (ii) collector - base junction.
- (I) Base emitter junction is always a forward biased so that current flows through it.
- (II) whereas collector - base junction is always reverse biased.



COEP TECHNOLOGICAL UNIVERSITY, PUNE

Wellesly Road, Shivajinagar, Pune - 411005

Q-8

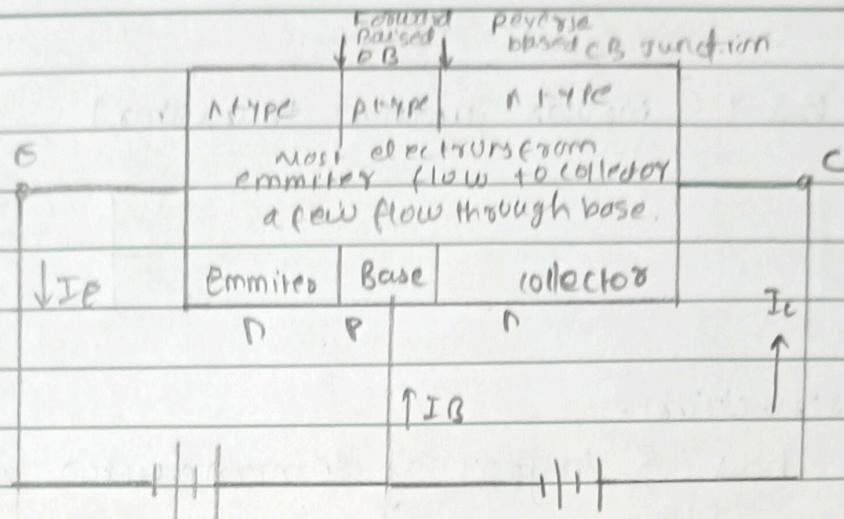

⇒ (i) EB Junction is a forward biased junction. Therefore the majority charge carriers from N type emmiter flow from emmiter to the base junction.

(ii) Only 2% of the electrons from the emmiter will recombine with holes in the base region because base is lightly doped.

(iii) Due to large CB bias voltage electrons will be pulled across the CB junction by positive terminal of collector.

(iv) They collector collects 98% of the electrons emitted by the emmiter.

The quantity of charge carriers crossing the emmiter to the base is controlled by base emmiter bias voltage.

⇒ emmiter and collector controlled by base collector - emmiter bias voltage



COEP TECHNOLOGICAL UNIVERSITY, PUNE

Wellesly Road, Shivajinagar, Pune - 411005


Q.9

An NPN or a PNP transistor can be used in 3 configurations.


- common base configuration (CB)
- common Emitter configuration (CE)
- common collector configuration (CC)

Diagrams. (For NPN transistors)


(i) common base configuration (CB)

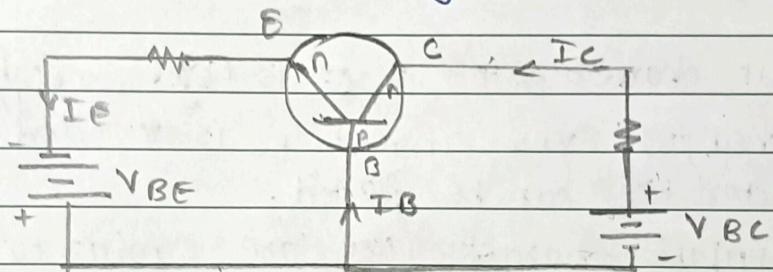

(ii) common Emitter configuration (CE)

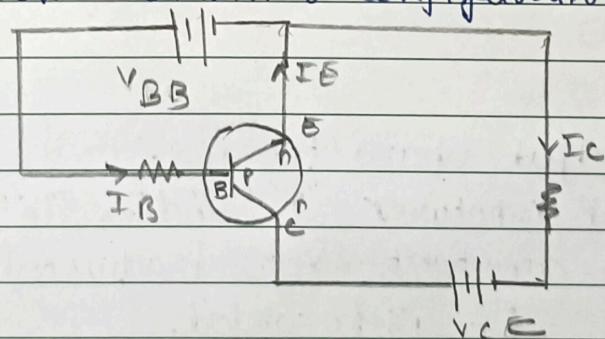

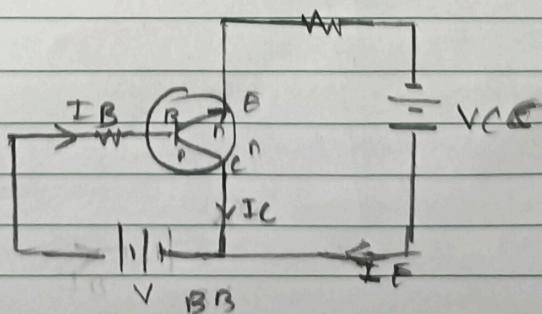(iii) common collector configuration (CC)






COEP TECHNOLOGICAL UNIVERSITY, PUNE

Wellesley Road, Shivajinagar, Pune - 411005

Q.10)

BJT in common emitter configuration.


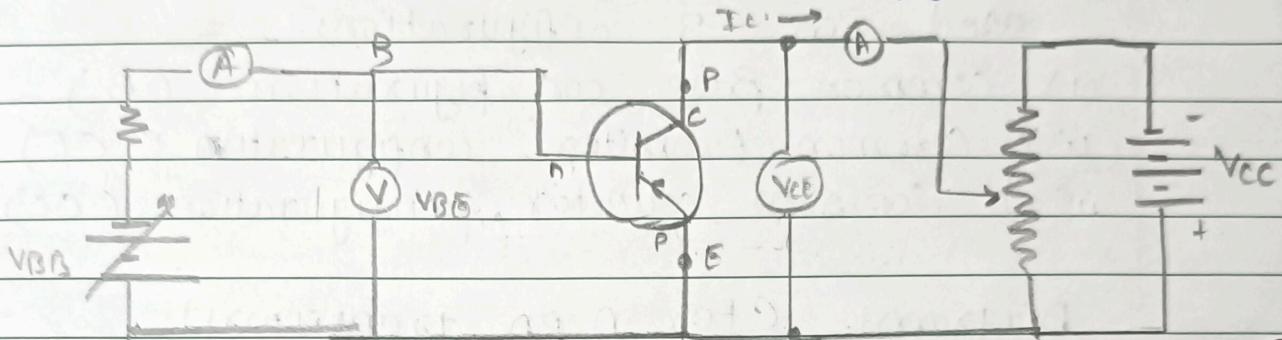


CE input characteristics. $V_{BB} = r_{in}$

- For input characteristics V_{CE} is kept constant
- By changing V_{BE} current I_B is recorded and the characteristics can be plotted.
- Input characteristics are similar to characteristics of forward biased p-n junction. The value of I_B is very small. in uA only.

\Rightarrow CE output characteristics.

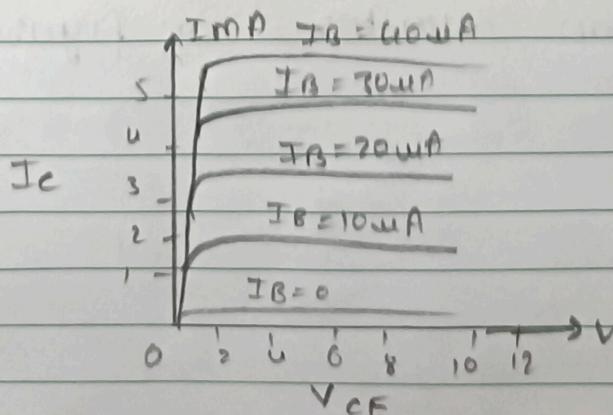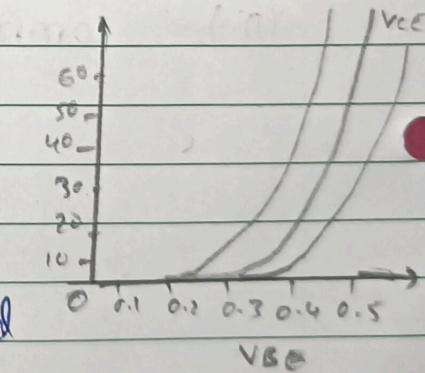- Output is between I_C and V_{CE} , I_B is kept constant. V_{CE} is adjusted and I_C is recorded.



current gain

$$\beta_{dc} = \frac{\Delta I_C}{\Delta I_B}$$


can be used as current amplifying device.



COEP TECHNOLOGICAL UNIVERSITY, PUNE

Wellesley Road, Shivajinagar, Pune - 411005

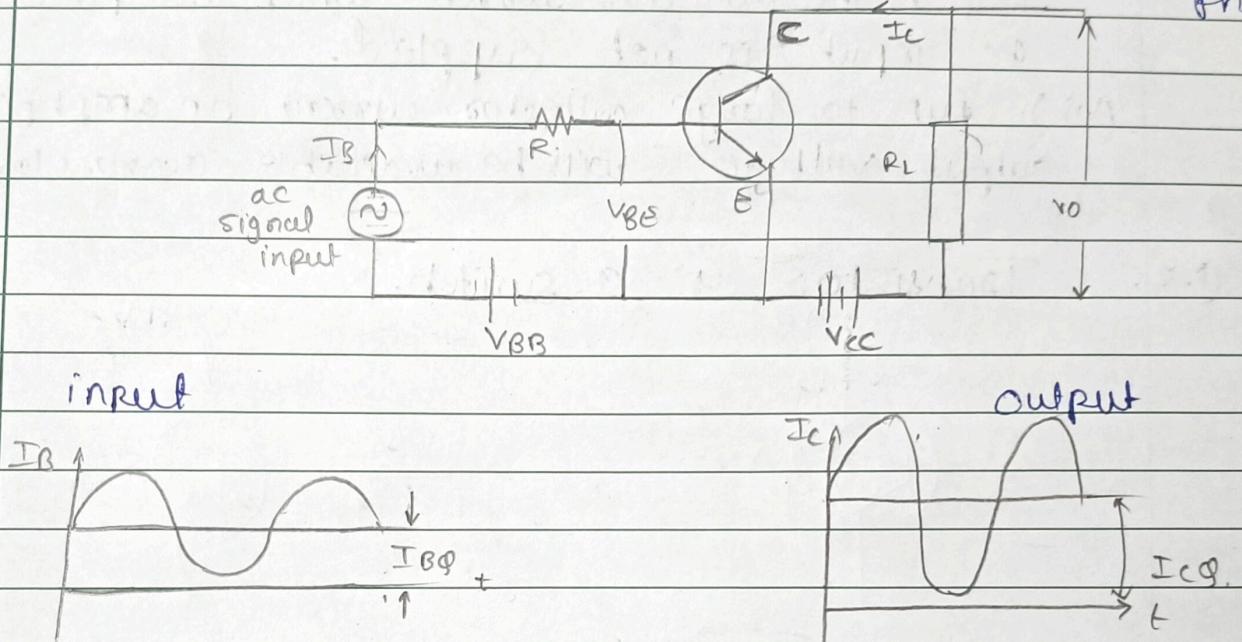- Q.11) \rightarrow Transistor as an amplifier. (Output 180°)
 \Rightarrow An (NPN) transistor in CE configuration. out of phase)



- \rightarrow (i) The AC signal is to be amplified is connected to the base circuit.
- (ii) the output is taken across resistance R_L in collector circuit
- (iii) The voltage V_{BE} is the summation of DC voltage V_{BB} and AC input v_i ; the DC voltage V_{CC} is a bias voltage.

- (iv) The magnitude of V_{BE} is such that it will always remain positively biased in both half cycles of input voltage.
- (v) $I_B = I_{BQ}(\text{dc}) + I_{AC}$

\Rightarrow if I_B is changed slightly large change in I_C occurs which flows through R_L



COEP TECHNOLOGICAL UNIVERSITY, PUNE



Wellesly Road, Shivajinagar, Pune - 411005

(vii) Amplified collector ac current is superimposed on the dc current I_C .

I_{CQ} is the collector current which will flow if ac input is not supplied.

(viii) Due to large collector current an amplified output voltage will be available across load.

Q.12. Transistor as a switch.

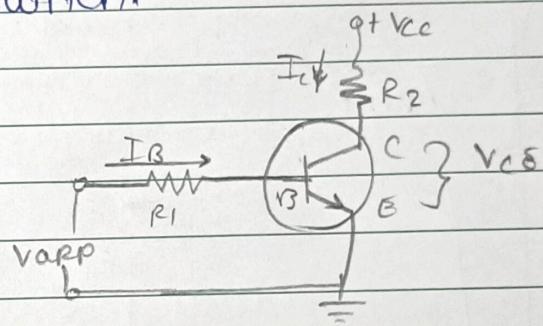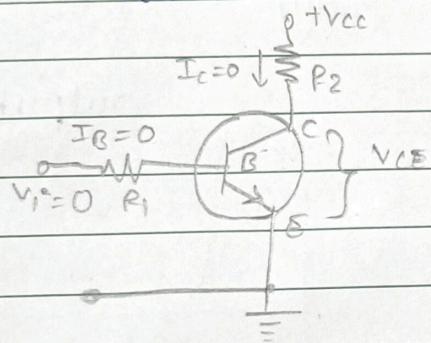

Off state of BJT

The base voltage is either at zero level or at an appropriate positive level when $V_i = 0$, $I_B = 0$ and $I_C = 0$.


On state of BJT

If V_i is at positive level and base current I_B is made high enough the transistor operates in saturation region.


The transistor is cut off and acts as an open switch.

Untersaturated condition
large collector current I_C flows and transistor operates as open switch.

Q.13) ① Half wave rectifiers circuit

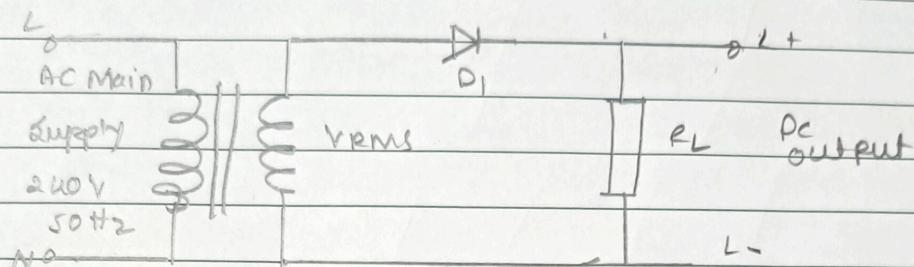


output waveform (input)

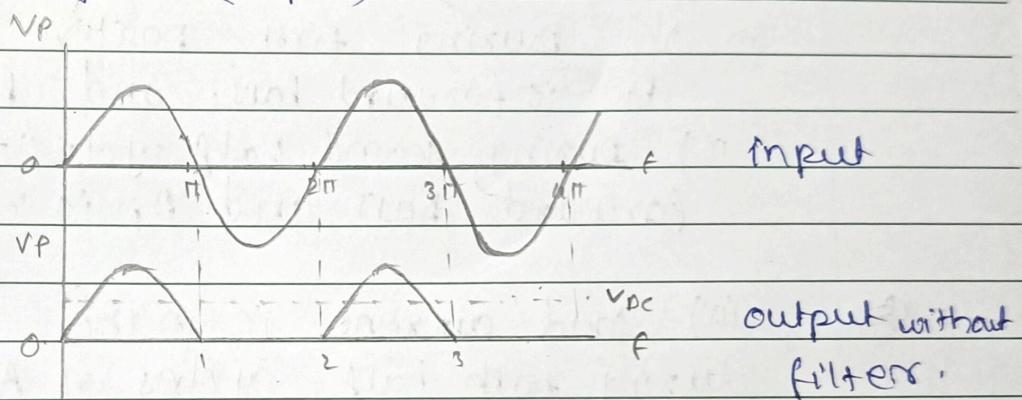


① Diode D_1 acts as forward biased during positive half cycle \therefore it is a p-N junction. It conducts electricity

② Diode D_1 acts as reversed bias and acts as an insulator. so the negative half cycle gets eliminated

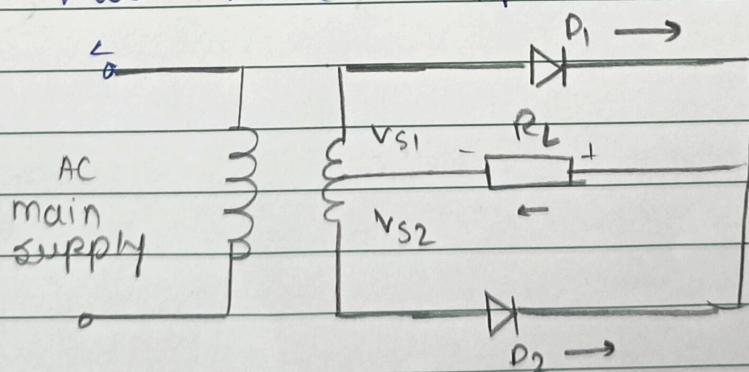Q.14) ② Full Wave Rectifier circuit. (centre tapped)



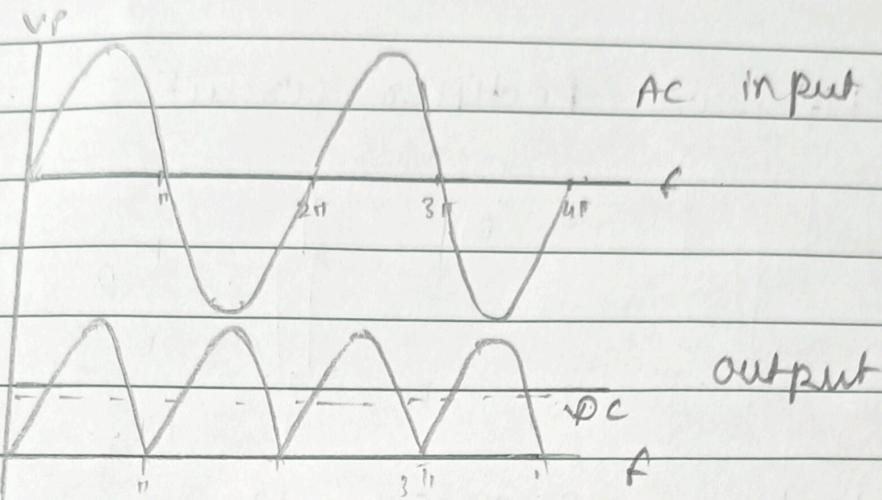

⇒ (i) During first positive half cycle
 D_1 is forward bias. and D_2 is reverse

(ii) During second half cycle (-ve) Diode D_2 is forward bias and D_1 is reverse bias.

~~(iii)~~ (iii) Load current is in the same direction during both half cycles of AC input,
 $DC \text{ output } V_{dc} = 0.9 \times V_{rms}$.

Ripple frequency = 2 times AC input freq.

peak inverse voltage \geq Peak inverse voltage across diode in reverse biased condition is equal to two times the peak value of secondary voltage.




COEP TECHNOLOGICAL UNIVERSITY, PUNE

Wellesly Road, Shivajinagar, Pune - 411005

O-15

Bridge Rectifier

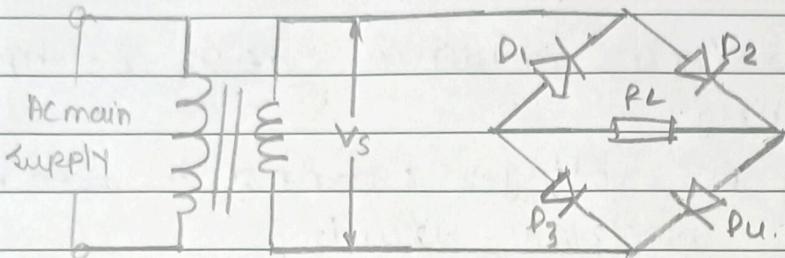

- It is a full wave rectifier.
- 4 Diodes are used
- no need of center tap.

(I)


(i) For positive half cycle secondary voltages D_2 and D_3 are forward biased.

(ii) For current flows through diode D_2 load resistance R_L and D_3 to the other end of the secondary.

(II)

(i) During negative half of the secondary voltage diode D_1 and D_4 are conducting.

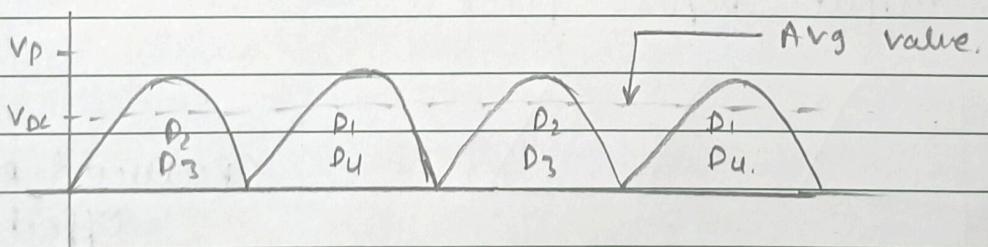(ii) The current flows through diode D_4 resistor R_L and diode D_1 to other end of the secondary



→ Output Ripple frequency is double of the input AC frequency.



COEP TECHNOLOGICAL UNIVERSITY, PUNE

Wellesly Road, Shivajinagar, Pune - 411005


Q.16

Filter in Rectified circuit.


- ⇒ (i) Output waveform obtained after rectifying is pulsating.
- (ii) Pulsating DC voltages cannot be used in most of the electronic circuits.
- (iii) The filters are used to Reduce pulsation in DC output of rectifiers are known as smoothing circuits or popularly as Ripple Filters.

An example of filter circuit.

(a) Capacitor Filter.

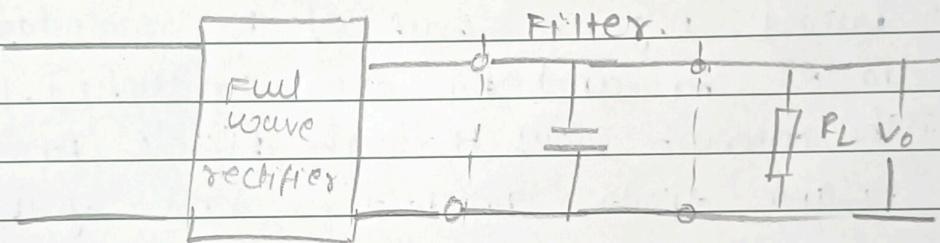

⇒ output Before filter .

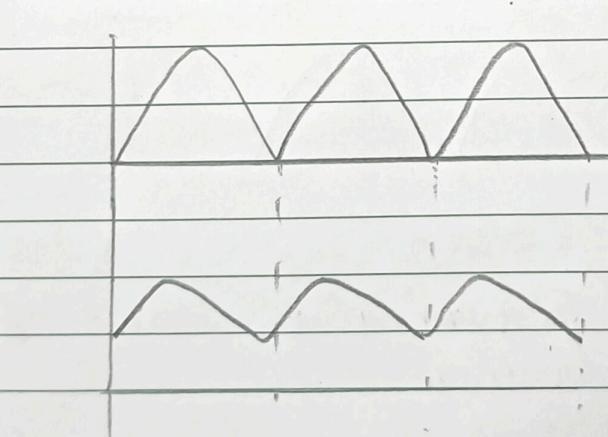

(Reduced ripple effect)

output with filter



COEP TECHNOLOGICAL UNIVERSITY, PUNE

Wellesly Road, Shivajinagar, Pune - 411005

Q.17 For $\beta_{dc} = ?$

(i) $\alpha_{dc} = 0.9$

we know that.

$$I_E = I_C + I_B \quad \text{--- (1)}$$

$$\beta_{dc} = \frac{I_C}{I_B} \quad \alpha_{dc} = \frac{I_C}{I_E} \Rightarrow k = \frac{I_B}{I_E}$$

$\alpha_{dc} =$

divide (1) with I_C on both sides,

$$\Rightarrow \frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

$$\therefore \beta = \frac{\alpha}{1-\alpha} = \frac{0.9}{0.1} = 9$$

(ii) $\Rightarrow k = \frac{0.98}{0.02} = 0.98$

$$\beta_{dc} = \frac{0.98}{0.02} = 49$$

(iii) $\beta_{dc} = \frac{0.99}{0.01} = 99$



COEP TECHNOLOGICAL UNIVERSITY, PUNE

Wellesly Road, Shivajinagar, Pune - 411005

Q.18

$$I_E = ?$$

$$\beta = 50$$

$$I_B = 20 \mu A$$

$$\beta = \frac{I_C}{I_B}$$

$$I_C = 50 \times 20 \times 10^{-6} = 1 \text{ mA}$$

$$\begin{aligned} \text{Now, } I_E &= I_C + I_B \\ &= 10^{-3} + 20 \times 10^{-6} \\ &= 10^{-3} + 0.02 \times 10^{-3} \\ \boxed{I_E &= 1.02 \text{ mA}}. \end{aligned}$$