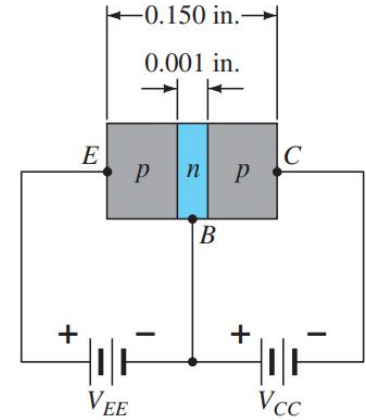


Bipolar Junction Transistor

By Dr. Saiyma Fatima Raza

Transistor Construction

- The transistor is a three-layer semiconductor device consisting of either two n - and one p -type layers of material or two p - and one n -type layers of material.
- The former is called an npn transistor , and the latter is called a pnp transistor.
- The emitter layer is heavily doped, with the base and collector only lightly doped.
- The outer layers have widths much greater than the sandwiched p - or n -type material.
- For the transistors shown in Fig. the ratio of the total width to that of the center layer is $0.150/0.001 = 150:1$.
- The doping of the sandwiched layer is also considerably less than that of the outer layers (typically, 1:10 or less).
- This lower doping level decreases the conductivity (increases the resistance) of this material by limiting the number of “free” carriers.



Transistor operation

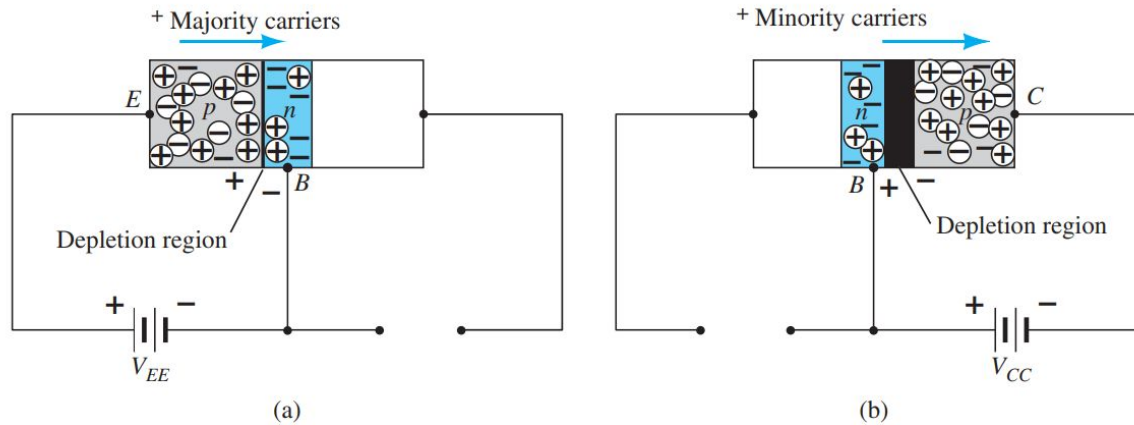


FIG. 3.4

Biasing a transistor: (a) forward-bias; (b) reverse-bias.

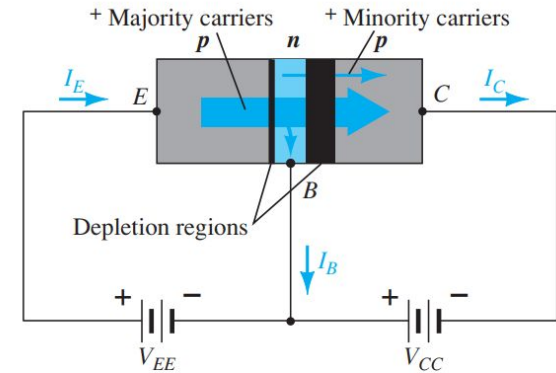


FIG. 3.5

Majority and minority carrier flow of a pnp transistor.

Contd...



- Applying Kirchhoff's current law to the transistor as if it were a single node, we obtain

$$I_E = I_C + I_B$$

- The collector current, however, comprises two components—the majority and the minority carriers.
- The minority-current component is called the leakage current and is given the symbol I_{CO} (I_C current with emitter terminal Open). The collector current, therefore, is determined in total by

$$I_C = I_{C_{\text{majority}}} + I_{CO_{\text{minority}}}$$

Common Base Configuration

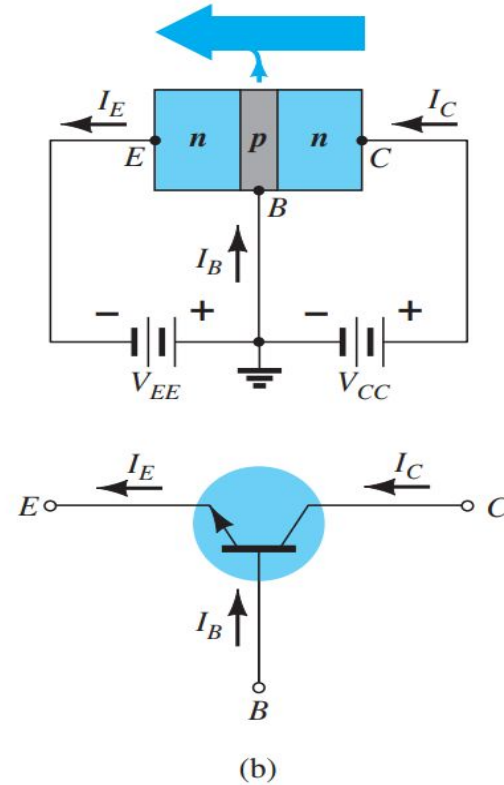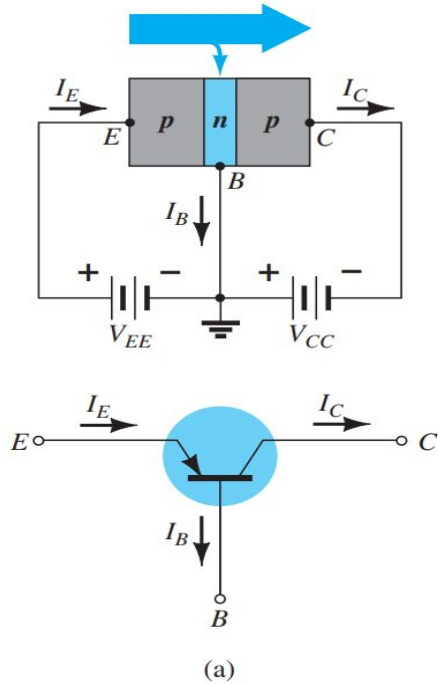

Contd...

- Two sets of characteristics are required for 3 terminal device—one for the driving point or input parameters and the other for the output side.
- The input set for the common-base amplifier relates an input current (I_E) to an input voltage (V_{BE}) for various levels of output voltage (V_{CB}).
- $V_{BE} = 0.7$ for ON state.

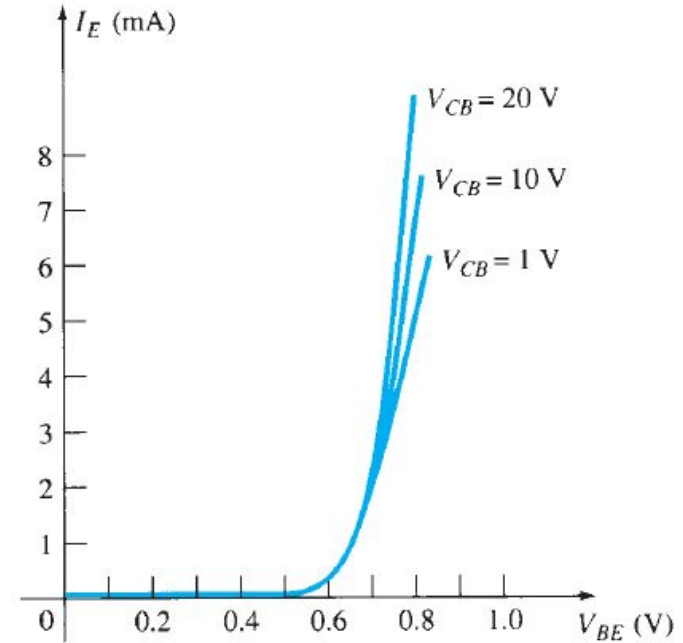


Fig. Input or driving point characteristics for a common-base silicon transistor amplifier.

Contd...

- The output set relates an output current (I_C) to an output voltage (V_{CB}) for various levels of input current (I_E)
- The output or collector set of characteristics has three basic regions of interest: **the active , cutoff , and saturation region.**

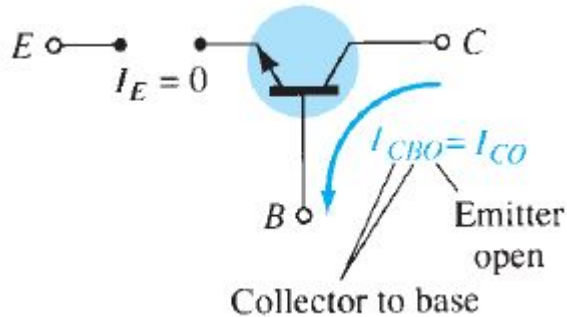


Fig. Reverse saturation current

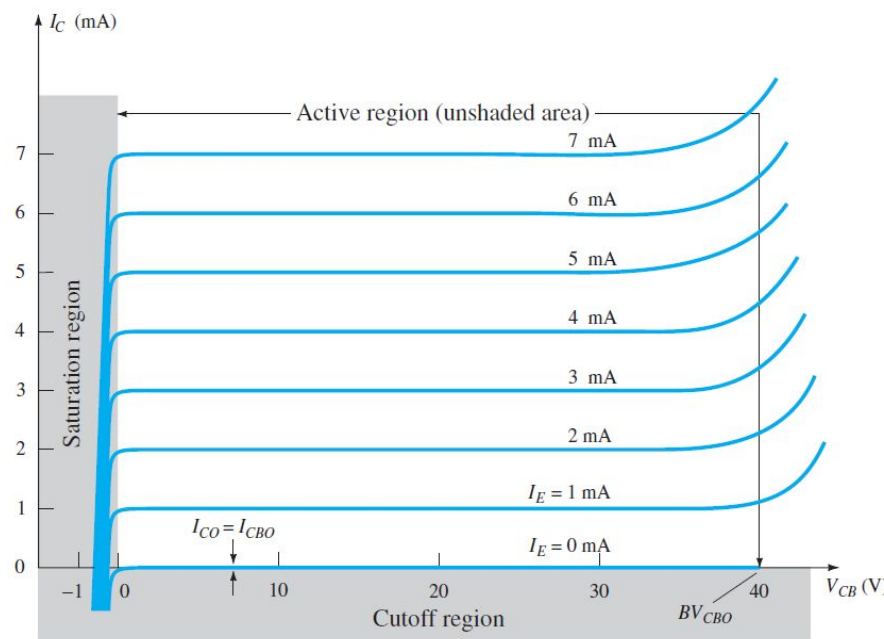


Fig. Output or collector characteristics for a common-base transistor amplifier.

Common Base DC Current Gain (α_{dc})

- Ratio of output current to input current is called current gain of a transistor.
- In the dc mode the levels of I_C and I_E due to the majority carriers are related by a quantity called alpha and defined by the following equation:

$$\alpha_{dc} = \frac{I_C}{I_E}$$

- α ranges from : 0.90 to -0.998

$$I_C = I_{C_{\text{majority}}} + I_{CO_{\text{minority}}} \longrightarrow I_C = \alpha I_E + I_{CBO}$$

Common Base AC Current Gain (α_{ac})

- The ac alpha is formally called the common-base , short-circuit , amplification factor.
- For ac situations where the point of operation moves on the characteristic curve, an ac alpha is defined by

$$\alpha_{ac} = \left. \frac{\Delta I_C}{\Delta I_E} \right|_{V_{CB} = \text{constant}}$$



Common-Emitter Configuration

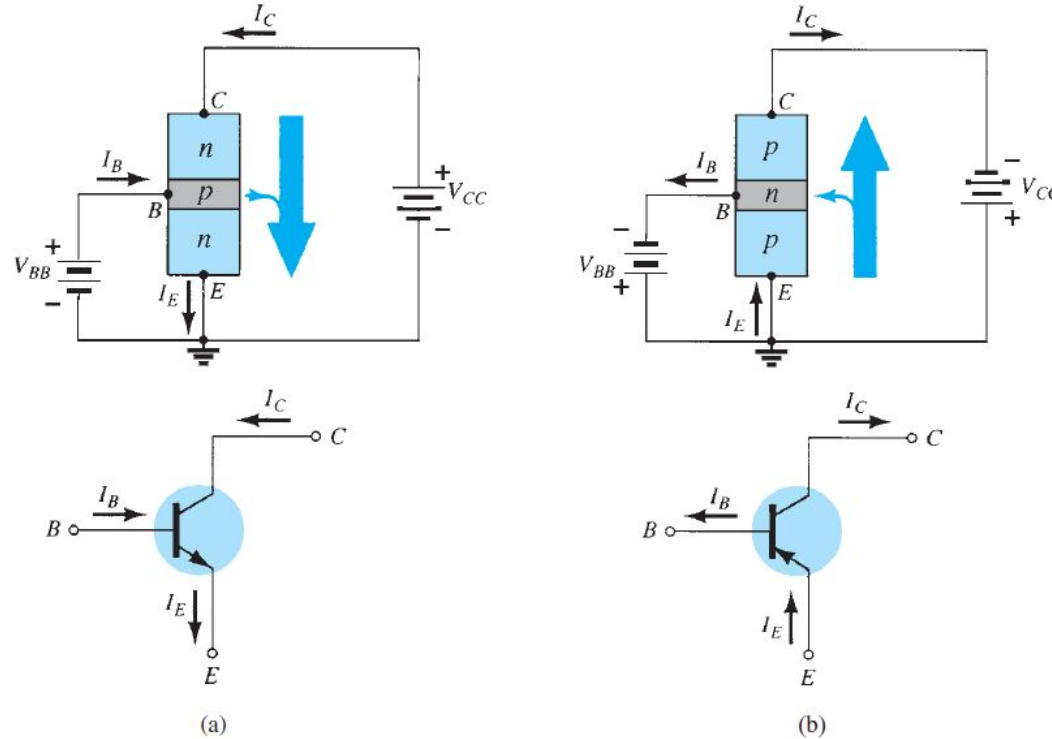


FIG. 3.12

Notation and symbols used with the common-emitter configuration: (a) npn transistor; (b) pnp transistor.

Contd...

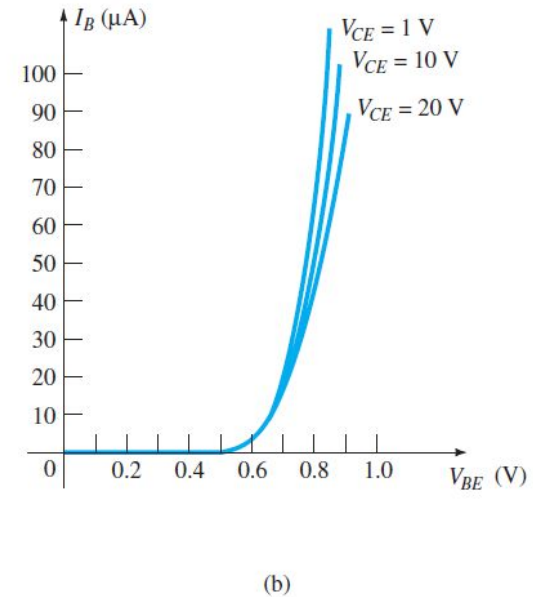
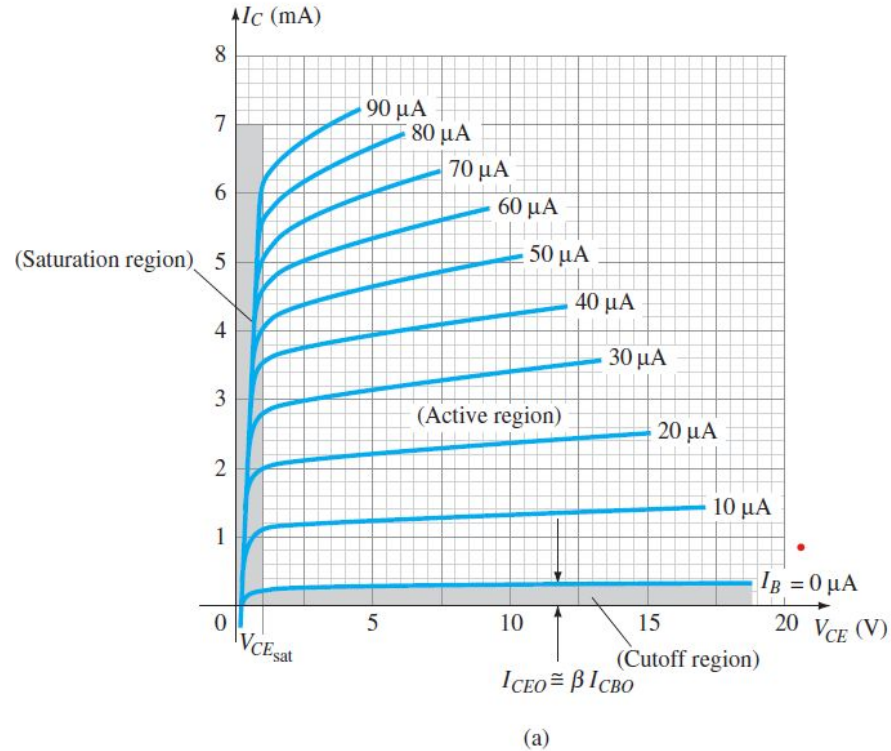


FIG. 3.13

Characteristics of a silicon transistor in the common-emitter configuration: (a) collector characteristics; (b) base characteristics.

Contd...

- In the active region of a common-emitter amplifier, the base-emitter junction is forward-biased, whereas the collector-base junction is reverse-biased.
- In collector characteristics that I_C is not equal to zero when I_B is zero.
- The reason for this difference in collector characteristics can be derived through:

$$I_C = \alpha I_E + I_{CBO}$$

$$I_C = \alpha(I_C + I_B) + I_{CBO}$$

$$I_C = \frac{\alpha I_B}{1 - \alpha} + \frac{I_{CBO}}{1 - \alpha}$$



Contd...

- The collector current defined by the condition $I_B = 0$ mA is I_{CEO}
- For linear (least distortion) amplification purposes, cutoff for the common-emitter configuration will be defined by $I_C = I_{CEO}$.

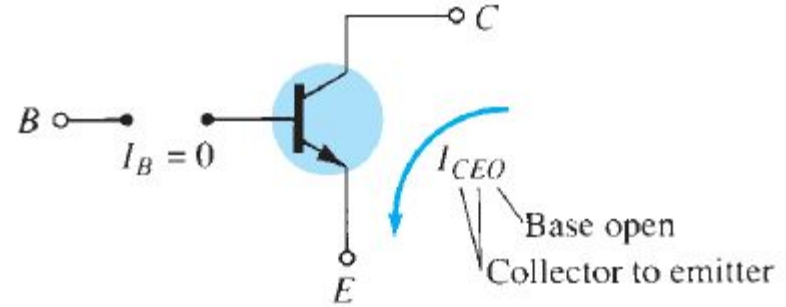


FIG. 3.14

Circuit conditions related to I_{CEO} .

$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha} \Big|_{I_B = 0 \mu A}$$

Common Emitter DC/AC Current Gain (β_{dc}/β_{ac})

- Ratio of collector (output) current to base (input) current

$$\beta_{dc} = \frac{I_C}{I_B}$$

- The formal name β_{ac} for is common-emitter , forward-current , amplification factor . Since the collector current is usually the output current for a common-emitter configuration and the base current is the input current
-



Relation between α_{dc} and β_{dc}

- A relationship can be developed between β and α using the basic relationships introduced
- Using $\beta = I_C/I_B$, we have $I_B = I_C/\beta$, and from $\alpha = I_C/I_E$ we have $I_E = I_C/\alpha$.
Substituting into

$$I_E = I_C + I_B$$

$$\frac{I_C}{\alpha} = I_C + \frac{I_C}{\beta}$$

or

so that

or

$$\frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

$$\beta = \alpha\beta + \alpha = (\beta + 1)\alpha$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

Contd...

In addition, recall that

$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha}$$

but using an equivalence of

$$\frac{1}{1 - \alpha} = \beta + 1$$

derived from the above, we find that

$$I_{CEO} = (\beta + 1)I_{CBO}$$

or

$$I_{CEO} \cong \beta I_{CBO}$$

and since

$$\begin{aligned} I_E &= I_C + I_B \\ &= \beta I_B + I_B \end{aligned}$$

we have

$$I_E = (\beta + 1)I_B$$

$$I_C = \beta I_B$$



Common Collector Configuration

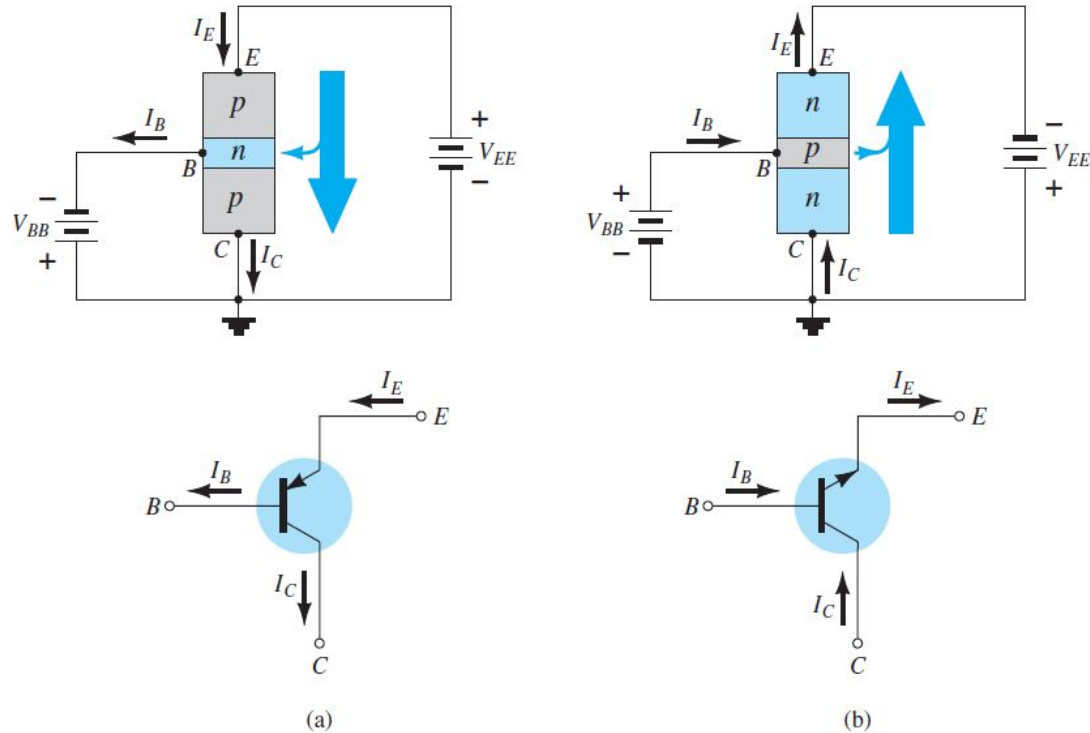


FIG. 3.20

Notation and symbols used with the common-collector configuration: (a) pnp transistor; (b) npn transistor.

Contd...

The common-collector configuration is used primarily for impedance-matching purposes since it has a high input impedance and low output impedance, opposite to that of the common-base and common emitter configurations.

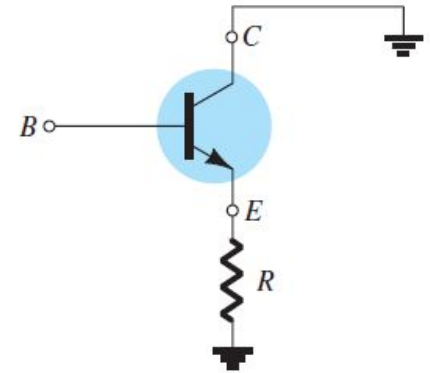


FIG. 3.21

*Common-collector configuration
used for impedance-matching
purposes.*

Limits of Operation

- For each transistor there is a region of operation on the characteristics that will ensure that the maximum ratings are not being exceeded and the output signal exhibits minimum distortion.
- The maximum dissipation level is defined by the following equation:

$$P_{C_{\max}} = V_{CE}I_C$$

- The cutoff region is defined as that region below $I_C = I_{CEO}$.



Contd...

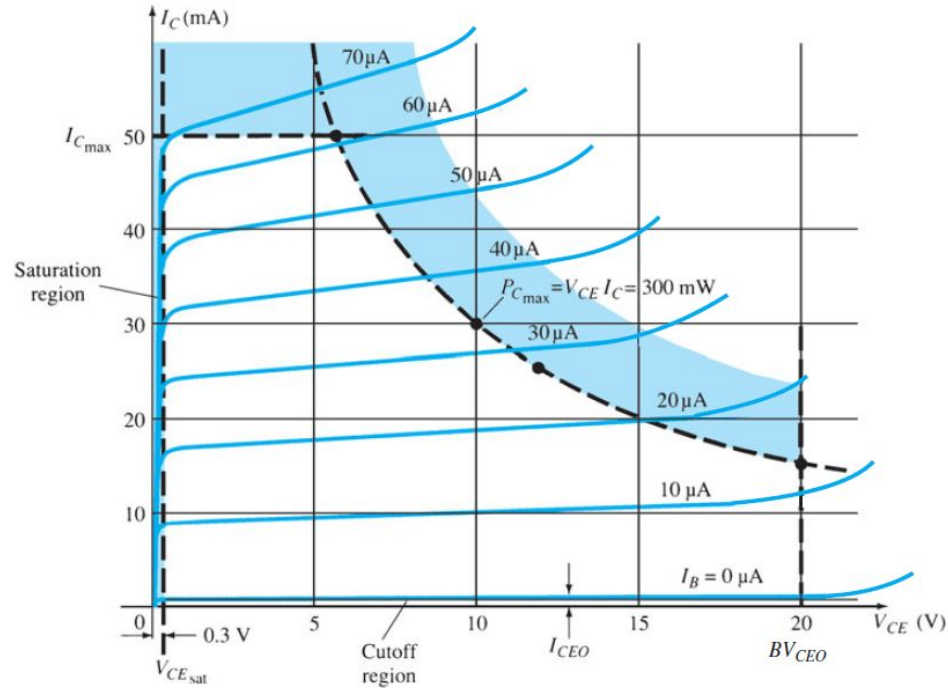


FIG. 3.22

Defining the linear (undistorted) region of operation for a transistor.

$$\begin{aligned} I_{CEO} &\leq I_C \leq I_{C_{\max}} \\ V_{CE_{\text{sat}}} &\leq V_{CE} \leq V_{CE_{\max}} \\ V_{CE} I_C &\leq P_{C_{\max}} \end{aligned}$$